

APTRANSCO AEE / ELECTRICAL

2026 MASTER FORMULA & REVISION HANDBOOK

CBT Examination | 100 Marks | No Negative Marking

Exam Date: 26 August 2026

Core Electrical 70 Marks + Common Section 30 Marks

Every Formula | Every Shortcut | Every Trap | Theory Key Points

Previous-Exam Repeated Topics Highlighted

High-Density | Exam-Focused | Mobile-Readable | Print-Ready

TABLE OF CONTENTS

1. Official Exam Pattern & Syllabus Checklist
2. Master Constants, Conversions & Quick-Reference Tables
3. ELECTRIC CIRCUITS (DC, AC, Network Theorems, RLC, Transients, 3-Phase, Two-Port, Harmonics)
4. ELECTRICAL MACHINES (Transformer, DC Machines, Induction Motor, Synchronous Machines)
5. POWER SYSTEMS (Generation, Transmission, Cables, Insulators, PU, Faults, Protection, Stability)
6. CONTROL SYSTEMS (Transfer Function, Stability, Root Locus, Bode, Compensators)
7. UTILIZATION (Heating, Welding, Electric Traction)
8. MEASUREMENTS (Bridges, Instruments, CRO, Q-Meter, Digital Instruments)
9. ANALOG & DIGITAL ELECTRONICS (Diodes, BJT, FET, Op-Amp, Logic Gates, Flip-Flops, ADC/DAC)
10. POWER ELECTRONICS & DRIVES (SCR, Rectifiers, Choppers, Inverters, Drives)
11. QUANTITATIVE APTITUDE (All Formulas & Shortcuts)
12. REASONING SHORTCUTS
13. ENGLISH GRAMMAR RULES & SHORTCUTS
14. COMPUTER KNOWLEDGE KEY FACTS
15. GENERAL AWARENESS REVISION FRAMEWORK
16. 100 MOST COMMON FORMULA TRAPS
17. MASTER FORMULA TABLES (Quick-Reference)
18. HIGH-PRIORITY FORMULA LIST (Top 80 Formulas)
19. FORMULA-TO-QUESTION-TYPE MAPPING
20. SIX-DAY REVISION PLAN (21-26 Aug 2026)
21. FINAL 2-HOUR EXAM STRATEGY
22. ONE-PAGE ULTRA-REVISION SHEET
23. PREVIOUS-EXAM THEORY KEY POINTS

1. OFFICIAL EXAM PATTERN & SYLLABUS CHECKLIST

SECTION	SUBJECT	MARKS	QUESTIONS
Core EE	Electric Circuits	~10	10
Core EE	Electrical Machines	~15	15
Core EE	Power Systems	~18	18
Core EE	Utilization & Control Systems	~12	12
Core EE	Measurements	~5-8	5-8
Core EE	Analog & Digital Electronics	~5-8	5-8
Core EE	Power Electronics & Drives	~5-7	5-7
Common	General Intelligence & Reasoning	5	5
Common	General Awareness	7	7
Common	English Language	5	5
Common	Quantitative Aptitude	8	8
Common	Computer Knowledge	5	5
TOTAL		100	100

KEY: No negative marking = Attempt EVERY question. Even a random guess has 25% chance.

KEY: 1 mark per question. Each question carries equal weight.

KEY: Duration: 2 hours (120 minutes) for 100 questions = 72 seconds per question average.

2. MASTER CONSTANTS, CONVERSIONS & QUICK-REFERENCE

FUNDAMENTAL CONSTANTS

CONSTANT	SYMBOL	VALUE	UNIT
Pi	pi	3.14159265	
Root 2	root(2)	1.41421	
Root 3	root(3)	1.73205	
1/root(3)	1/root(3)	0.57735	
Permeability of free space	mu_0	4pi x 10^-7	H/m
Permittivity of free space	epsilon_0	8.854 x 10^-12	F/m
Speed of light	c	3 x 10^8	m/s
Electron charge	e	1.602 x 10^-19	C
Boltzmann constant	k	1.381 x 10^-23	J/K
Thermal voltage (27C)	V_T	26 mV	V
Planck constant	h	6.626 x 10^-34	J-s

SI PREFIXES

PREFIX	SYMBOL	FACTOR	PREFIX	SYMBOL	FACTOR
tera	T	10¹²	milli	m	10⁻³
giga	G	10⁹	micro	mu	10⁻⁶
mega	M	10⁶	nano	n	10⁻⁹
kilo	k	10³	pico	p	10⁻¹²
hecto	h	10²	femto	f	10⁻¹⁵

TRIGONOMETRIC VALUES (Memorize!)

ANGLE	sin	cos	tan
0 deg	0	1	0
30 deg	0.5	0.866	0.577
45 deg	0.707	0.707	1
60 deg	0.866	0.5	1.732
90 deg	1	0	infinity

DEGREE-RADIAN CONVERSION

1 radian = 180/pi = 57.296 deg | 1 deg = pi/180 = 0.01745 rad
30 deg = pi/6 | 45 deg = pi/4 | 60 deg = pi/3 | 90 deg = pi/2 | 180 deg = pi | 360 deg = 2pi

AC WAVEFORM VALUES (SINE WAVE)

PARAMETER	FORMULA	VALUE (for Vm)	REMARKS
Peak (Vm)	Vm	Vm	Maximum instantaneous
Peak-to-Peak	Vpp	2Vm	Total swing
RMS	Vm/root(2)	0.707 Vm	Equivalent DC heating
Average (full-cycle)		0	Zero for full cycle

PARAMETER	FORMULA	VALUE (for V_m)	REMARKS
Average (half-cycle)	$2V_m/\pi$	$0.637 V_m$	Half-wave rectified
Form Factor	V_{rms}/V_{avg}	1.11	Always 1.11 for sine
Crest/Peak Factor	V_m/V_{rms}	1.414 (root2)	Always root(2) for sine

TRAP: Form Factor and Crest Factor values change for non-sinusoidal waveforms. 1.11 and 1.414 are ONLY for pure sine.

3. ELECTRIC CIRCUITS

3.1 DC CIRCUITS FUNDAMENTALS

Ohm's Law [FFF]

$$V = I \times R$$

Where: V = Voltage (V), I = Current (A), R = Resistance (Ohm)

Use when: All linear resistive circuits

Condition: Valid only for ohmic (linear) materials. Not valid for diodes, thermistors.

Trap: Do not apply Ohm's law to non-linear elements. V/I for a diode is NOT resistance.

Shortcut: If any two of V, I, R are known, third is found instantly.

Kirchhoff's Current Law (KCL) [FFF]

Sum of currents at a node = 0 (currents entering = currents leaving)

Where: I = current (A). Convention: entering = positive, leaving = negative.

Use when: At every node in any circuit (DC or AC)

Condition: Based on conservation of charge. Always valid.

Trap: Sign convention must be consistent. Forgetting direction causes wrong equations.

Shortcut: For 2 branches at a node: $I_{in} = I_{out}$ directly.

Kirchhoff's Voltage Law (KVL) [FFF]

Sum of voltages around any closed loop = 0

Where: V = voltage (V). Convention: rise = positive, drop = negative.

Use when: Around any closed loop in any circuit

Condition: Based on conservation of energy. Always valid.

Trap: Polarity of voltage across a component depends on assumed current direction.

Shortcut: Start from one point, traverse loop, return to same point. Sum = 0.

Series Resistance [FFF]

$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_n$$

Where: R in Ohm. Same current flows through all resistors.

Use when: Resistors connected end-to-end (same current path)

Condition: Current is same in all. Voltage divides. $R_{eq} > R_{largest}$.

Trap: Never use parallel formula for series connection.

Shortcut: For n identical resistors: $R_{eq} = nR$.

Parallel Resistance [FFF]

$$1/R_{eq} = 1/R_1 + 1/R_2 + \dots \quad | \quad \text{For 2: } R_{eq} = R_1 \cdot R_2 / (R_1 + R_2)$$

Where: R in Ohm. Same voltage across all resistors.

Use when: Resistors connected across same two nodes (same voltage)

Condition: Voltage same across all. Current divides. $R_{eq} < R_{smallest}$.

Trap: Do NOT add resistances directly. Must use reciprocal formula.

Shortcut: For n identical: $R_{eq} = R/n$. For 2 equal: $R_{eq} = R/2$.

Voltage Division Rule (VDR) [FFF]

$$V_k = V_{total} \times R_k / (R_1 + R_2 + \dots + R_n)$$

Where: V_k = voltage across k-th resistor. V_{total} = source voltage.

Use when: Series circuit with multiple resistors and a voltage source

Condition: Only valid when NO current is drawn from the output terminal (open-circuit).

Trap: Fails completely if a load is connected across the output. Must account for parallel combination.

Shortcut: For 2 resistors: $V_1 = V \times R_1 / (R_1 + R_2)$, $V_2 = V \times R_2 / (R_1 + R_2)$.

Current Division Rule (CDR) [FFF]

$$I_k = I_{total} \times R_{other} / (R_k + R_{other}) \quad [\text{for 2 parallel } R]$$

Where: I_k = current through k-th branch. I_{total} = total current entering node.

Use when: Parallel circuit with current source or known total current

Condition: Current is INVERSELY proportional to resistance. More current flows through smaller R.

Trap: Current divider uses OPPOSITE resistance in numerator (not same as voltage divider).

Shortcut: For n equal parallel resistors: $I_k = I_{\text{total}} / n$.

Power (DC) [FFF]

$$P = VI = I^2R = V^2/R$$

Where: P = power (W), V = voltage (V), I = current (A), R = resistance (Ohm)

Use when: All DC resistive circuits. Choose form based on known quantities.

Condition: $P = I^2R$ and $P = V^2/R$ only for resistive elements. $P = VI$ is general.

Trap: Using $P = V^2/R$ with wrong V (e.g. source V instead of element V) is common.

Shortcut: Energy: $E = P \times t$ (Joules) = $P \times t/3600$ (Wh). 1 kWh = 3.6 MJ = 1 Unit of electricity.

Star-Delta (Y-Delta) Conversion [FF]

Delta to Star: $R_a = R_{ab}R_{ca}/(R_{ab}+R_{bc}+R_{ca})$ [and cyclic]

Star to Delta: $R_{ab} = R_aR_b/R_c + R_a + R_b$ [and cyclic]

Where: R_a, R_b, R_c = star arms. R_{ab}, R_{bc}, R_{ca} = delta arms.

Use when: When circuit cannot be simplified by series/parallel alone

Condition: For balanced (equal R): $R_{\text{star}} = R_{\text{delta}}/3$ and $R_{\text{delta}} = 3R_{\text{star}}$.

Trap: Confusing numerator/denominator in conversion. Delta-to-Star: product of adjacent / sum of all.

Shortcut: Balanced case shortcut: $R_Y = R_{\text{Delta}}/3$ solves 90% of exam questions.

Source Transformation [FF]

Voltage source V_s in series with R <--> Current source $I_s = V_s/R$ in parallel with R

Where: V_s = source voltage, I_s = source current, R = internal resistance.

Use when: Simplifying circuits for node/mesh analysis

Condition: Ideal voltage source ($R=0$) cannot be converted. Ideal current source ($R=\infty$) cannot be converted.

Trap: Direction of current source must match polarity of voltage source (current flows from - to + inside source).

Shortcut: Useful to convert all sources to same type before analysis.

KEY: [THEORY] Supernode: formed when voltage source connects two non-reference nodes. Write KCL for supernode boundary + constraint equation $V_1 - V_2 = V_s$.

KEY: [THEORY] Supermesh: formed when current source is common to two meshes. Write KVL around combined mesh + constraint equation $I_1 - I_2 = I_s$.

3.2 NETWORK GRAPH THEORY

Graph Theory Relationships [FF]

$b = l + (n-1)$ where b =branches, l =links, n =nodes

Where: b =total branches, n =total nodes, l =links (co-tree branches).

Use when: Determining number of independent KVL/KCL equations

Condition: Tree has $(n-1)$ branches. Links = $b-(n-1)$. Independent KVL equations = l . Independent KCL equations = $n-1$.

Trap: Forgetting that tree must connect ALL nodes without forming any loop.

Shortcut: No. of mesh equations = links = $b-n+1$. No. of node equations = $n-1$.

KEY: [THEORY] Tree: connected subgraph containing all nodes but no loops. Co-tree: remaining branches (links).

KEY: [THEORY] Incidence matrix (A): rows=nodes, cols=branches. Entry +1 if branch leaves node, -1 if enters, 0 otherwise.

KEY: [THEORY] Tie-set matrix: Each link forms exactly one fundamental loop with tree branches.

KEY: [THEORY] Cut-set matrix: Each tree branch defines exactly one fundamental cut-set.

3.3 NETWORK THEOREMS

Thevenin's Theorem [FFF]

V_{Th} = Open-circuit voltage at terminals

R_{Th} = Equivalent resistance seen from terminals (sources killed)

$I_L = V_{Th} / (R_{Th} + R_L)$

Where: V_{Th} (V), R_{Th} (Ohm), R_L = load resistance, I_L = load current.

Use when: Finding current/voltage across a specific load in a complex circuit

Condition: Kill independent sources: short voltage sources, open current sources. Dependent sources remain active.

Trap: Common error: shorting dependent sources or opening them. Dependent sources are NEVER killed.

Shortcut: $V_{Th} = V_{oc}$ (open-circuit voltage). $R_{Th} = V_{oc}/I_{sc}$ (if dependent sources present).

Norton's Theorem [FFF]

I_N = Short-circuit current at terminals

$R_N = R_{Th}$ (same equivalent resistance)

$I_L = I_N \times R_N / (R_N + R_L)$

Where: I_N (A), R_N (Ohm). Norton is current-source equivalent of Thevenin.

Use when: When current source representation is more convenient

Condition: $R_N = R_{Th}$ always. $I_N = V_{Th}/R_{Th}$.

Trap: I_N is found by shorting the load terminals and finding current through the short.

Shortcut: Convert between Thevenin and Norton: $V_{Th} = I_N \times R_N$, $I_N = V_{Th}/R_{Th}$.

Maximum Power Transfer (DC) [FFF]

Condition: $R_L = R_{Th}$

$P_{max} = V_{Th}^2 / (4 \times R_{Th})$

Efficiency at max power = 50%

Where: R_L = load, R_{Th} = Thevenin resistance, P_{max} = maximum power to load.

Use when: Designing load for maximum power absorption

Condition: At max power, half the power is dissipated in R_{Th} . Efficiency = 50% (not desirable for power systems).

Trap: Max power transfer != max efficiency. Power systems optimize efficiency, not max power transfer.

Shortcut: $P_{max} = V_{Th}^2/(4R_{Th}) = I_N^2 \times R_{Th}/4$. Quick formula.

Maximum Power Transfer (AC) [FFF]

$Z_L = Z_{Th}^*$ (complex conjugate)

If $Z_{Th} = R_{Th} + jX_{Th}$, then $Z_L = R_{Th} - jX_{Th}$

If only R_L variable: $R_L = |Z_{Th}| = \sqrt{R_{Th}^2 + X_{Th}^2}$

Where: Z_L = load impedance, Z_{Th} = Thevenin impedance, * = conjugate.

Use when: AC circuits with complex impedances

Condition: Full conjugate match: $R_L = R_{Th}$ and $X_L = -X_{Th}$. If only R adjustable: $R_L = |Z_{Th}|$.

Trap: DC: $R_L = R_{Th}$. AC: $Z_L = Z_{Th}^*$ (conjugate). Confusing these is very common.

Shortcut: For purely resistive Thevenin, AC and DC conditions are identical.

Superposition Theorem [FF]

Response = Sum of individual responses due to each independent source acting alone

Where: Each source acts alone while others are killed (V-source shorted, I-source opened).

Use when: Linear circuits with multiple independent sources

Condition: Valid ONLY for linear circuits. Cannot be used for power (P is non-linear).

Trap: Cannot superpose power! Must find voltage/current first, then calculate power from total.

Shortcut: Dependent sources are NEVER killed. They remain active in every sub-circuit.

KEY: [THEORY] Reciprocity Theorem: In a linear bilateral network with single source, if source and response are interchanged, ratio V/I remains same.

KEY: [THEORY] Substitution Theorem: Any branch can be replaced by an independent source equal to the voltage across it (or current through it).

KEY: [THEORY] Millman's Theorem: $V = (V_1/R_1 + V_2/R_2 + \dots + V_n/R_n) / (1/R_1 + 1/R_2 + \dots + 1/R_n)$. Quick for parallel voltage sources.

KEY: [THEORY] Tellegen's Theorem: Sum of power delivered by all branches = 0 (conservation of energy).

3.4 AC FUNDAMENTALS & IMPEDANCE

Sinusoidal Voltage/Current [FFF]

$$v(t) = V_m \sin(\omega t + \phi) \quad | \quad i(t) = I_m \sin(\omega t + \theta)$$

Where: V_m =peak voltage, I_m =peak current, $\omega=2\pi f$ (rad/s), f =frequency (Hz), ϕ, θ =phase angles.

Use when: All AC circuit analysis

Condition: $\omega = 2\pi f = 2\pi/T$. T = time period (s). $f = 1/T$.

Trap: Confusing ω (rad/s) with f (Hz). Always check if question gives ω or f .

Shortcut: If $v = V_m \sin(\omega t)$ and $i = I_m \sin(\omega t - \phi)$, current LAGS voltage by ϕ .

Impedance (Z) [FFF]

$$Z = R + jX = |Z| \angle(\phi)$$

$$|Z| = \sqrt{R^2 + X^2}$$

$$\phi = \arctan(X/R)$$

Where: R =resistance, X =reactance ($X_L - X_C$), $|Z|$ =magnitude, ϕ =angle. All in Ohm.

Use when: AC circuit analysis in phasor/frequency domain

Condition: $X_L = \omega L = 2\pi f L$ (positive, inductive). $X_C = 1/(\omega C) = 1/(2\pi f C)$ (negative for net reactance).

Trap: X is NET reactance: $X = X_L - X_C$. Sign determines lagging (+) or leading (-).

Shortcut: For series: $Z_{\text{total}} = Z_1 + Z_2 + \dots$ For parallel: $1/Z_{\text{total}} = 1/Z_1 + 1/Z_2 + \dots$

Admittance (Y) [FF]

$$Y = 1/Z = G + jB$$

$$G = R/|Z|^2 \text{ (conductance, Siemens)}$$

$$B = -X/|Z|^2 \text{ (susceptance, Siemens)}$$

Where: Y =admittance (S), G =conductance (S), B =susceptance (S).

Use when: Parallel AC circuit analysis (easier with admittance)

Condition: G is NOT simply $1/R$ when X is present. $G = R/(R^2 + X^2)$.

Trap: $G \neq 1/R$ in general. This is one of the most common errors in AC circuits.

Shortcut: For parallel: $Y_{\text{total}} = Y_1 + Y_2 + \dots$ (add directly).

AC Power Formulas [FFF]

$$P = VI \cos(\phi) \text{ [Active/Real power, W]}$$

$$Q = VI \sin(\phi) \text{ [Reactive power, VAR]}$$

$$S = VI = \sqrt{P^2 + Q^2} \text{ [Apparent power, VA]}$$

$$\text{Power Factor} = \cos(\phi) = P/S$$

Where: V, I are RMS values. ϕ = angle between V and I .

Use when: All AC power calculations. V and I MUST be RMS (not peak).

Condition: $P > 0$ always (absorbed). $Q > 0$ for lagging (inductive), $Q < 0$ for leading (capacitive).

Trap: Using peak values instead of RMS in power formulas (P would be 2x the correct value).

Shortcut: Power triangle: P (horizontal), Q (vertical), S (hypotenuse). $PF = \cos(\phi)$.

Complex Power [FF]

$$S = P + jQ = V \times I^* \text{ (} I^* = \text{conjugate of } I \text{)}$$

$$S = |I|^2 Z = |V|^2 / Z^*$$

Where: S = complex power (VA), V = phasor voltage, I^* = conjugate of phasor current.

Use when: Complete power analysis including direction of reactive power

Condition: Use conjugate of current, NOT current itself.

Trap: Forgetting to conjugate I . $S = V \times I^*$ not $V \times I$.

Shortcut: $|S|$ = apparent power. $\text{Real}(S) = P$. $\text{Imag}(S) = Q$.

3.5 RLC CIRCUITS, RESONANCE & Q-FACTOR

Series RLC Impedance [FFF]

$$Z = R + j(\omega L - 1/\omega C)$$

$$|Z| = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

Where: R (Ohm), L (H), C (F), $\omega = 2\pi f$.

Use when: Any series RLC circuit

Condition: If $\omega L > 1/\omega C$: inductive (lagging). If $\omega L < 1/\omega C$: capacitive (leading). If equal: resonance.

Trap: Net reactance is $(X_L - X_C)$, not $(X_L + X_C)$.

Shortcut: At resonance: $X_L = X_C$, $Z = R$ (minimum), $I = V/R$ (maximum).

Series Resonance [FFF]

$$f_r = 1 / (2\pi \sqrt{LC}) \quad | \quad \omega_r = 1/\sqrt{LC}$$

At resonance: $Z = R$ (min), $I = V/R$ (max)

$$Q = \omega_r L / R = 1/(\omega_r C R) = (1/R) \sqrt{L/C}$$

$$BW = f_r / Q = R / (2\pi L)$$

Half-power frequencies: $f_1 = f_r - BW/2$, $f_2 = f_r + BW/2$

Voltage magnification: $V_L = V_C = Q \times V_{source}$

Where: f_r =resonant freq (Hz), Q =quality factor, BW =bandwidth (Hz).

Use when: Filter design, frequency selection, voltage magnification

Condition: Higher Q = narrower bandwidth = sharper selectivity. V_L and V_C can be $> V_{source}$ ($Q > 1$).

Trap: At resonance, V_L and V_C are equal but OPPOSITE (cancel each other). $V_R = V_{source}$.

Shortcut: Quick: $Q = f_r / BW$. If Q and f_r known, $BW = f_r / Q$ immediately.

Parallel Resonance (Ideal) [FFF]

$$f_r = 1/(2\pi \sqrt{LC}) \quad [\text{same formula}]$$

At resonance: $Z = \text{infinity}$ (ideal) or $Z = L/(RC)$ (practical)

$$Q = R/(\omega_r L) = \omega_r C R = R \sqrt{C/L}$$

$$BW = f_r / Q$$

Current magnification: $I_L = I_C = Q \times I_{source}$

Where: For ideal parallel RLC. Practical: $Z_{max} = L/(RC)$.

Use when: Tank circuits, oscillators, signal selection

Condition: Parallel resonance: MAX impedance, MIN current. Opposite of series.

Trap: Q formula for parallel is INVERSE of series Q formula!

Shortcut: Series: $Q = \omega L / R$. Parallel: $Q = R / (\omega L)$. Don't swap them.

TRAP: SERIES resonance: $Z=\text{min}$, $I=\text{max}$, $Q=\omega L/R$. PARALLEL resonance: $Z=\text{max}$, $I=\text{min}$, $Q=R/\omega L$. Every quantity is opposite!

3.6 TRANSIENTS (FIRST & SECOND ORDER)

RL Circuit Transient [FFF]

Current rise: $i(t) = (V/R)(1 - e^{-t/\tau})$

Current decay: $i(t) = I_0 * e^{-t/\tau}$

Time constant: $\tau = L/R$ seconds

Where: V=source voltage, R=resistance, L=inductance, I_0 =initial current.

Use when: Switching ON/OFF an RL circuit

Condition: At $t=0$: $i=0$ (inductor opposes change). At $t=\infty$: $i=V/R$ (steady state). At $t=\tau$: $i=0.632*I_{\text{final}}$.

Trap: $\tau = L/R$ (not R/L). Larger L or smaller R = slower response.

Shortcut: After $5*\tau$, transient is essentially complete (>99%).

RC Circuit Transient [FFF]

Charging: $v_C(t) = V(1 - e^{-t/\tau})$

Discharging: $v_C(t) = V_0 * e^{-t/\tau}$

Time constant: $\tau = RC$ seconds

Where: V=source voltage, R=resistance, C=capacitance, V_0 =initial voltage.

Use when: Switching ON/OFF an RC circuit

Condition: At $t=0$: $v_C=0$ (capacitor is short). At $t=\infty$: $v_C=V$ (fully charged). At $t=\tau$: $v_C=0.632*V$.

Trap: $\tau = RC$ (not C/R). Capacitor voltage cannot change instantaneously.

Shortcut: After $5*\tau$, capacitor is >99% charged. Quick: $1\tau=63.2\%$, $2\tau=86.5\%$, $3\tau=95\%$, $5\tau=99.3\%$.

RLC Second-Order Circuit [FF]

Characteristic eq: $s^2 + 2*\alpha*s + \omega_0^2 = 0$

$\alpha = R/(2L)$ [series], $\omega_0 = 1/\sqrt{LC}$

Damping ratio: $\zeta = \alpha/\omega_0 = R/(2)*\sqrt{C/L}$

Where: α =damping coeff, ω_0 =undamped natural freq, ζ =damping ratio.

Use when: RLC circuits with switching or sudden changes

Condition: $\zeta < 1$: underdamped (oscillatory). $\zeta = 1$: critically damped. $\zeta > 1$: overdamped.

Trap: Confusing α and ω_0 formulas for series vs parallel RLC.

Shortcut: Underdamped: $\omega_d = \omega_0*\sqrt{1-\zeta^2}$. Overdamped: two real roots s_1, s_2 .

KEY: [THEORY] Initial conditions: $i_L(0^-) = i_L(0^+)$ [inductor current continuous]. $v_C(0^-) = v_C(0^+)$ [capacitor voltage continuous].

KEY: [THEORY] Complete response = Natural response + Forced response. Natural dies out; forced is steady-state.

3.7 MUTUAL INDUCTANCE & COUPLING

Mutual Inductance [FF]

$M = k \cdot \sqrt{L_1 \cdot L_2}$

$k = M / \sqrt{L_1 \cdot L_2}$ [coupling coefficient, $0 \leq k \leq 1$]

Where: M=mutual inductance (H), L1,L2=self-inductances (H), k=coupling coefficient.

Use when: Coupled coils, transformers

Condition: k=1: perfect coupling (ideal transformer). k=0: no coupling. Practical transformers: k=0.95-0.99.

Trap: M can never exceed $\sqrt{L_1 \cdot L_2}$. If computed $M > \sqrt{L_1 \cdot L_2}$, check calculation.

Shortcut: For tightly wound coils on same core: k is close to 1.

Series Aiding / Opposing [FF]

Aiding (dots same end): $L_{eq} = L_1 + L_2 + 2M$

Opposing (dots opposite): $L_{eq} = L_1 + L_2 - 2M$

Where: L_{eq} = equivalent inductance when two coupled coils are in series.

Use when: Finding equivalent inductance of coupled coils in series

Condition: Aiding: fluxes add (larger L). Opposing: fluxes subtract (smaller L).

Trap: Sign of M depends on dot convention. Aiding (+2M), Opposing (-2M).

Shortcut: $M = (L_{aiding} - L_{opposing})/4$. Quick way to find M experimentally.

3.8 TWO-PORT NETWORKS

PARAMETER	EQUATIONS	RECIPROCITY	SYMMETRY
Z parameters	$V_1 = Z_{11} \cdot I_1 + Z_{12} \cdot I_2, V_2 = Z_{21} \cdot I_1 + Z_{22} \cdot I_2$	$Z_{12} = Z_{21}$	$Z_{11} = Z_{22}$
Y parameters	$I_1 = Y_{11} \cdot V_1 + Y_{12} \cdot V_2, I_2 = Y_{21} \cdot V_1 + Y_{22} \cdot V_2$	$Y_{12} = Y_{21}$	$Y_{11} = Y_{22}$
h parameters	$V_1 = h_{11} \cdot I_1 + h_{12} \cdot V_2, I_2 = h_{21} \cdot I_1 + h_{22} \cdot V_2$	$h_{12} = -h_{21}$	$h_{11} \cdot h_{22} - h_{12} \cdot h_{21} = 1$
ABCD params	$V_1 = A \cdot V_2 - B \cdot I_2, I_1 = C \cdot V_2 - D \cdot I_2$	$AD - BC = 1$	$A = D$

KEY: Series connection: Z-parameters add. Parallel: Y-parameters add. Cascade: ABCD multiply.

TRAP: ABCD cascade: multiply matrices in ORDER of connection (left to right). Not commutative if networks differ.

3.9 THREE-PHASE CIRCUITS

QUANTITY	STAR (Y)	DELTA (Triangle)
Line Voltage V _L	$\sqrt{3} \times V_{ph}$	V _{ph}
Phase Voltage V _{ph}	$V_L / \sqrt{3}$	V _L
Line Current I _L	I _{ph}	$\sqrt{3} \times I_{ph}$
Phase Current I _{ph}	I _L	$I_L / \sqrt{3}$
Total Active Power P	$\sqrt{3} \times V_L \times I_L \times \cos(\phi)$	$\sqrt{3} \times V_L \times I_L \times \cos(\phi)$
Total Reactive Power Q	$\sqrt{3} \times V_L \times I_L \times \sin(\phi)$	$\sqrt{3} \times V_L \times I_L \times \sin(\phi)$
Total Apparent Power S	$\sqrt{3} \times V_L \times I_L$	$\sqrt{3} \times V_L \times I_L$
Impedance relation	$Z_Y = Z_{Delta} / 3$	$Z_{Delta} = 3 \times Z_Y$

Two-Wattmeter Method [FFF]

$P_{total} = W1 + W2$

$\tan(\phi) = \sqrt{3} \times (W1 - W2) / (W1 + W2)$

$\cos(\phi) = \text{power factor}$

Where: W1, W2 = readings of two wattmeters. ϕ = power factor angle.

Use when: Measuring 3-phase power with only 2 wattmeters (balanced or unbalanced)

Condition: At PF=0.5: one wattmeter reads zero. At PF<0.5: one reads negative (reverse connections).

Trap: If PF < 0.5, one wattmeter gives NEGATIVE reading. Must reverse connections and subtract.

Shortcut: $PF = \cos[\arctan(\sqrt{3} \times (W1-W2)/(W1+W2))]$. Quick PF from wattmeter readings.

TRAP: 3-phase power = $\sqrt{3} \times V_L \times I_L \times \cos(\phi)$. The $\sqrt{3}$ factor is ALWAYS present regardless of Star or Delta.

TRAP: Line-Phase relationships are DIFFERENT for Star and Delta. In Star: $V_L = \sqrt{3} \times V_{ph}$, $I_L = I_{ph}$. In Delta: $V_L = V_{ph}$, $I_L = \sqrt{3} \times I_{ph}$.

3.10 HARMONICS IN AC CIRCUITS

RMS of Distorted Waveform [FF]

$$V_{rms} = \sqrt{V_{dc}^2 + V1_{rms}^2 + V2_{rms}^2 + V3_{rms}^2 + \dots}$$

Where: V_{dc} =DC component, $V1$ =fundamental RMS, $V2, V3, \dots$ =harmonic RMS values.

Use when: Finding total RMS when waveform has harmonics

Condition: Each harmonic contributes independently to total RMS (Parseval's theorem).

Trap: Cannot simply add RMS values. Must square, add, then take square root.

Shortcut: $THD = \sqrt{V2^2 + V3^2 + \dots} / V1 \times 100\%$. Measure of distortion.

KEY: [THEORY] In 3-phase balanced systems: 3rd harmonics (triplen: 3,6,9,...) are zero-sequence and circulate in Delta, not in line currents.

KEY: [THEORY] Fundamental: positive sequence. 2nd harmonic: negative sequence. 3rd: zero sequence. Pattern repeats.

KEY: [THEORY] Only odd harmonics exist in symmetrical waveforms (half-wave symmetry).

4. ELECTRICAL MACHINES

4.1 TRANSFORMER

EMF Equation [FFF]

$$E = 4.44 f N \Phi_m \text{ (Volts RMS)}$$

$$E1 = 4.44 f N1 \Phi_m \quad | \quad E2 = 4.44 f N2 \Phi_m$$

Where: f =frequency (Hz), N =turns, Φ_m =maximum flux (Wb). $4.44 = 4 \times 1.11 = 2\pi / (\sqrt{2} \times \pi / \sqrt{2})$.

Use when: Finding EMF of any winding of transformer or alternator

Condition: This gives RMS value. Φ_m is PEAK flux, not RMS.

Trap: 4.44 is for sinusoidal flux. For square wave: constant is 4.0. Confusing these in MCQs.

Shortcut: $E1/E2 = N1/N2$ directly (ratio of EMFs = ratio of turns).

Transformation Ratio [FFF]

$$K = N2/N1 = V2/V1 = I1/I2$$

Step-up: $K > 1$ ($V2 > V1$). **Step-down:** $K < 1$ ($V2 < V1$).

Where: K =transformation ratio, N =turns, V =voltage, I =current.

Use when: All transformer calculations

Condition: Current ratio is INVERSE of voltage ratio. $V1 \times I1 = V2 \times I2$ (power conservation for ideal).

Trap: $K = N2/N1$ (secondary/primary). Some texts define $K = N1/N2$. Check definition in question.

Shortcut: VA rating is same on both sides: $V1 \times I1 = V2 \times I2$.

Referred Impedance [FF]

$$Z2_{referred_to_primary} = Z2/K^2$$

$$Z1_{referred_to_secondary} = Z1 \times K^2$$

$$R_{eq1} = R1 + R2/K^2 \quad | \quad X_{eq1} = X1 + X2/K^2$$

Where: Z =impedance, $K = N2/N1$, R =resistance, X =reactance.

Use when: Equivalent circuit calculations, referred to one side

Condition: When referring to primary: divide secondary quantities by K^2 . To secondary: multiply primary by K^2 .

Trap: Using K instead of K^2 for impedance referral. Impedance scales as turns-ratio SQUARED.

Shortcut: $R_{eq} = R1 + R2'$ (referred). $X_{eq} = X1 + X2'$ (referred). $Z_{eq} = \sqrt{R_{eq}^2 + X_{eq}^2}$.

Voltage Regulation [FFF]

$$VR\% = (V_{no_load} - V_{full_load}) / V_{full_load} \times 100$$

$$\text{Approx: } VR\% = (I2 \times R_{eq2} \times \cos(\phi) + I2 \times X_{eq2} \times \sin(\phi)) / V2 \times 100 \text{ [lagging]}$$

$$VR\% = (I2 \times R_{eq2} \times \cos(\phi) - I2 \times X_{eq2} \times \sin(\phi)) / V2 \times 100 \text{ [leading]}$$

Where: VR =voltage regulation (%), $I2$ =load current, R_{eq2}, X_{eq2} =equivalent impedance referred to secondary.

Use when: Determining how much voltage drops under load

Condition: Positive VR = voltage drops (lagging loads, usually). Negative VR possible with leading loads (capacitive).

Trap: SIGN: + for lagging PF, - for leading PF. Most common MCQ error.

Shortcut: At UPF: $VR = I \times R_{eq} / V$ only (X term vanishes). At zero PF lag: $VR = I \times X_{eq} / V$ only.

Transformer Efficiency [FFF]

$$\eta = \text{Output} / (\text{Output} + \text{Losses}) \times 100$$

$$\eta = (x \cdot S \cdot \cos(\phi)) / (x \cdot S \cdot \cos(\phi) + P_i + x^2 \cdot P_{cu_FL}) \times 100$$

where x = fraction of full load ($x=1$ at FL, $x=0.5$ at half load)

$$\text{Max efficiency when: } x^2 \cdot P_{cu_FL} = P_i \Rightarrow x = \sqrt{P_i / P_{cu_FL}}$$

Where: η =efficiency, S =VA rating, P_i =iron/core loss (constant), P_{cu_FL} =full-load copper loss, x =loading fraction.

Use when: All efficiency calculations

Condition: Core loss is CONSTANT at all loads (depends on voltage/frequency only). Copper loss varies as x^2 .

Trap: Max efficiency does NOT occur at full load. It occurs when Cu loss = Core loss.

Shortcut: At max η : load fraction $x = \sqrt{P_i / P_{cu_FL}}$. If $P_i=100W$, $P_{cu}=400W$: $x=\sqrt{100/400}=0.5$ (half load).

All-Day Efficiency [FF]

$$\eta_{allday} = \text{Total energy output in 24h} / \text{Total energy input in 24h}$$

$$\text{Energy}_{input} = \text{Energy}_{output} + \text{Core}_{loss} \cdot 24 + \sum (x_i^2 \cdot P_{cu} \cdot t_i)$$

Where: Used for distribution transformers (loaded lightly most of the time).

Use when: Distribution transformers that are energized 24 hours

Condition: Core loss occurs for all 24 hours. Copper loss only during loading periods.

Trap: Core loss for 24h, NOT just loading hours. This is the key insight.

Shortcut: Minimize core loss for better all-day efficiency (use high-grade steel).

OC and SC Test Results [FFF]

OC Test (on LV side): W_{oc} =Core loss, I_{oc} =no-load current

$$\cos(\phi_{i0}) = W_{oc} / (V_{oc} \cdot I_{oc})$$

$$I_w = I_{oc} \cdot \cos(\phi_{i0}), I_m = I_{oc} \cdot \sin(\phi_{i0})$$

$$R_0 = V_{oc} / I_w, X_0 = V_{oc} / I_m$$

SC Test (on HV side): W_{sc} =Cu loss (at I_{sc}), $Z_{eq}=V_{sc}/I_{sc}$

$$R_{eq} = W_{sc} / I_{sc}^2, X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2}$$

Where: OC: measures core loss and magnetizing parameters. SC: measures copper loss and impedance.

Use when: Determining equivalent circuit parameters

Condition: OC on LV side (safe, low voltage). SC on HV side (low current needed). Both at rated conditions.

Trap: Confusing which test gives which loss. OC=Core loss. SC=Copper loss. NEVER reversed.

Shortcut: From SC: $Z_{eq} = V_{sc} / I_{sc}$, $R_{eq} = W_{sc} / I_{sc}^2$, $X_{eq} = \sqrt{Z^2 - R^2}$.

Autotransformer [FF]

$$kVA_{transferred} = S \cdot (1 - 1/K) \text{ [step-up: } K=V_2/V_1 > 1]$$

$$\text{Copper saving} = (1 - 1/K) \cdot 100\% \text{ [compared to 2-winding]}$$

$$kVA_{auto} / kVA_{2winding} = V_1 / (V_1 - V_2) \text{ [step-down, } V_1 > V_2]$$

Where: K =transformation ratio. Autotransformer has single winding.

Use when: When isolation is not needed and ratio is close to 1

Condition: Maximum saving when K is close to 1. No electrical isolation (safety concern).

Trap: Formula depends on step-up or step-down. Check K definition carefully.

Shortcut: Saving $\approx (1 - 1/K) \cdot 100$. For $K=2$: 50% saving. For $K=10$: 90% saving.

KEY: [THEORY-REPEATED] Parallel operation conditions: Same voltage ratio, same polarity, same phase sequence, same impedance percentage.

KEY: [THEORY-REPEATED] Buchholz relay: gas-actuated, only for oil-immersed transformers. Detects incipient faults.

KEY: [THEORY] Core losses = Hysteresis + Eddy current. P_h proportional to $f \cdot B_{max}^{1.6}$. P_e proportional to $f^2 \cdot B_{max}^2$.

KEY: [THEORY] Transformer oil: provides insulation AND cooling. BDV test checks oil quality (min 30kV for 2.5mm gap).

4.2 DC MACHINES

Generated EMF [FFF]

$$E = P \Phi Z N / (60 A)$$

where $A = P$ (lap winding), $A = 2$ (wave winding)

Simplified: $E = K_e \Phi N$

Where: P =poles, Φ =flux/pole (Wb), Z =total conductors, N =speed (rpm), A =parallel paths.

Use when: All DC generator and motor calculations

Condition: Lap winding: $A=P$ (high current, low voltage). Wave winding: $A=2$ (high voltage, low current).

Trap: Forgetting to use correct A value. Lap: $A=P$. Wave: $A=2$. Simplex only.

Shortcut: For given machine: E is directly proportional to ΦN . $E_1/E_2 = (\Phi_1 N_1)/(\Phi_2 N_2)$.

Torque Equation [FFF]

$$T = P \Phi Z I_a / (2 \pi A) \text{ [N-m]}$$

Simplified: $T = K_t \Phi I_a$

Also: $T = E I_a / (2 \pi N / 60) = E I_a / \omega$

Where: T =torque (N-m), I_a =armature current (A), ω =angular speed (rad/s).

Use when: Motor torque and mechanical power calculations

Condition: Torque depends on Φ and I_a , NOT on speed. Same current and flux = same torque at any speed.

Trap: Torque is NOT proportional to speed. T proportional to ΦI_a only.

Shortcut: $P_{\text{mech}} = T \omega = E_b I_a$.

Motor Equations (Shunt) [FFF]

$$V = E_b + I_a R_a \text{ [motor: } V > E_b]$$

$$I_L = I_a + I_f \text{ [line current]}$$

$$I_f = V/R_f \text{ [field current, constant if } V \text{ constant]}$$

$$\text{Speed: } N = (V - I_a R_a) / (K_e \Phi)$$

Speed control: (a) Armature resistance, (b) Field flux, (c) Supply voltage

Where: V =terminal voltage, E_b =back EMF, I_a =armature current, R_a =armature resistance, I_f =field current, R_f =field resistance.

Use when: All DC shunt motor problems

Condition: Back EMF opposes supply voltage. $I_a = (V - E_b)/R_a$. At starting: $E_b=0$, so $I_a = V/R_a$ (very high).

Trap: Generator: $V = E - I_a R_a$ ($E > V$). Motor: $V = E_b + I_a R_a$ ($V > E_b$). Sign is crucial.

Shortcut: Starting current $I_{st} = V/R_a$ (dangerous). Starter adds resistance to limit I_{st} .

Motor Equations (Series) [FFF]

$$V = E_b + I_a (R_a + R_{se})$$

$$I_L = I_a = I_f \text{ [all in series]}$$

Φ proportional to I_a (before saturation)

T proportional to I_a^2 (before saturation)

N proportional to $1/I_a$ (after saturation, approximately)

Where: R_{se} =series field resistance. Since field is in series, $I_f = I_a$.

Use when: High starting torque applications (traction, cranes, hoists)

Condition: Never run series motor at no-load: speed becomes dangerously high (N proportional to $1/\Phi$, Φ drops).

Trap: Series motor MUST have mechanical load connected. No-load = runaway speed.

Shortcut: T proportional to I_a^2 gives high starting torque. Ideal for traction.

DC Machine Efficiency [FF]

$$\eta = \text{Output} / \text{Input} \times 100$$

Generator: $\eta = V I_L / (V I_L + \text{Total losses})$

Motor: $\eta = (V I_L - \text{Total losses}) / (V I_L)$

$$\text{Total losses} = \text{Cu}_{\text{loss}} + \text{Core}_{\text{loss}} + \text{Mechanical}_{\text{loss}} + \text{Stray}_{\text{loss}}$$

Condition for max efficiency: Variable losses = Constant losses

Where: $\text{Cu}_{\text{loss}} = I_a^2 R_a$ (variable). Core+Mech+Stray = constant losses.

Use when: Efficiency calculation and optimization

Condition: Max efficiency when variable loss = constant loss (same as transformer).

Trap: Swinburne test: no-load test gives constant losses. Cannot determine commutation or temperature rise.

Shortcut: Hopkinson (back-to-back) test: full-load test with minimum power from supply. Two identical machines.

KEY: [THEORY-REPEATED] Speed control of DC shunt motor: Armature resistance (below base speed), Field resistance (above base speed), Ward-Leonard (both directions).

KEY: [THEORY-REPEATED] Armature reaction: cross-magnetizing effect shifts MNA, causes commutation problems. Interpoles/compensating windings used.

KEY: [THEORY] Commutation: process of current reversal in armature coil. Linear commutation ideal. Interpoles improve commutation.

KEY: [THEORY] Characteristics: Shunt motor=approximately constant speed. Series motor=variable speed, high starting torque. Compound=combination.

4.3 THREE-PHASE INDUCTION MOTOR

Synchronous Speed [FFF]

$$N_s = 120 \cdot f / P \text{ (rpm)}$$

where f =supply frequency (Hz), P =number of poles

Where: N_s =synchronous speed (rpm). Rotor always runs BELOW N_s (motoring mode).

Use when: All induction motor calculations. First step in any IM problem.

Condition: At 50 Hz: $2P=3000$, $4P=1500$, $6P=1000$, $8P=750$, $10P=600$, $12P=500$ rpm.

Trap: $N_s = 120f/P$, NOT $60f/P$. The 120 accounts for rev/min conversion.

Shortcut: Memorize standard speeds at 50 Hz for quick solving.

Slip [FFF]

$$s = (N_s - N_r) / N_s = (N_s - N_r) / N_s$$

$$N_r = N_s(1-s) \text{ [rotor speed]}$$

Slip at no-load: $s \approx 0.01-0.02$ (1-2%)

Slip at full-load: $s \approx 0.03-0.05$ (3-5%)

Where: s =slip (fraction, dimensionless), N_r =rotor speed (rpm).

Use when: Finding rotor speed, frequency, and losses

Condition: $s=0$: rotor at synchronous speed (no torque). $s=1$: rotor standstill (starting).

Trap: Use slip as FRACTION (0.04) in formulas, NOT percentage (4%). Most common error.

Shortcut: If $N_s=1500$, $N_r=1440$: $s = (1500-1440)/1500 = 0.04$ (4%).

Rotor Frequency [FFF]

$$f_r = s \cdot f$$

where f =supply frequency, s =slip

Where: f_r =rotor frequency (Hz). At standstill: $f_r=f$. At synchronous speed: $f_r=0$.

Use when: Rotor circuit analysis, rotor reactance calculation

Condition: Rotor reactance at slip s : $X_r(s) = s \cdot X_r(\text{standstill})$. Rotor impedance changes with slip.

Trap: At full load ($s=0.04$, $f=50\text{Hz}$): $f_r = 0.04 \cdot 50 = 2$ Hz only. Very low frequency.

Shortcut: Rotor reactance = $s \cdot X_2$. Rotor impedance = $R_2 + j s \cdot X_2$.

Power Flow (Air-gap, Mechanical, Losses) [FFF]

$$\text{Input Power } P_{in} = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos(\phi)$$

Stator losses: Stator Cu loss + Stator core loss

$$\text{Air-gap power: } P_{ag} = P_{in} - \text{Stator losses}$$

$$\text{Rotor Cu loss: } P_{rcu} = s \cdot P_{ag}$$

$$\text{Gross mechanical power: } P_{mech} = (1-s) \cdot P_{ag}$$

$$\text{Output} = P_{mech} - \text{Mechanical losses}$$

$$\text{CRITICAL RATIO: } P_{ag} : P_{rcu} : P_{mech} = 1 : s : (1-s)$$

Where: P_{ag} =air-gap power (power crossing air gap from stator to rotor).

Use when: All IM power and efficiency problems. This ratio is the MOST TESTED concept.

Condition: The ratio $1:s:(1-s)$ holds always. If $P_{ag}=100\text{kW}$ and $s=0.04$: $P_{rcu}=4\text{kW}$, $P_{mech}=96\text{kW}$.

Trap: Rotor Cu loss = $s \cdot P_{ag}$. NOT $s \cdot P_{input}$. Must subtract stator losses first.

Shortcut: Quick: $P_{rcu}/P_{mech} = s/(1-s)$. If rotor Cu loss and slip known, find mechanical power instantly.

Torque [FFF]

$$T = P_{ag} / \omega_{s} = P_{ag} / (2\pi \cdot N_s / 60)$$

$$T = (3 \cdot V^2 \cdot R_2 / s) / (2\pi \cdot N_s \cdot [(R_1 + R_2/s)^2 + (X_1 + X_2)^2])$$

$$\text{Starting torque (s=1): } T_{st} = (3 \cdot V^2 \cdot R_2) / (2\pi \cdot N_s \cdot [(R_1 + R_2)^2 + (X_1 + X_2)^2])$$

Where: T =torque (N-m), ω_s =synchronous angular speed (rad/s).

Use when: Torque calculation at any slip

Condition: Torque proportional to V^2 . If voltage halved, torque becomes 1/4.

Trap: T proportional to V^2 , NOT V . Half voltage = quarter torque, not half.

Shortcut: T_{start} with external rotor resistance R_{ext} : add R_{ext} to R_2 in the formula.

Maximum Torque & Condition [FFF]

$$\text{Condition: } s_m = R_2 / \sqrt{R_1^2 + (X_1 + X_2)^2} \approx R_2 / X_2 \text{ (if } R_1 \text{ negligible)}$$

$$T_{max} = (3 \cdot V^2) / (4\pi \cdot N_s \cdot [R_1 + \sqrt{R_1^2 + (X_1 + X_2)^2}])$$

$$\text{Approx: } T_{max} \approx 3 \cdot V^2 / (4\pi \cdot N_s \cdot (X_1 + X_2))$$

T_max is INDEPENDENT of R2. Adding R2 changes s_m but NOT T_max.

$$T_{st}/T_{max} = 2*s_m*R2 / (s_m^2 + R2^2/X2^2) \text{ [approximate]}$$

Where: s_m=slip at max torque. T_max depends on V^2 and X, not R2.

Use when: Finding slip at max torque, max torque value, starting torque ratio

Condition: Adding rotor resistance: s_m increases (max torque occurs at higher slip = lower speed) but T_max stays same.

Trap: T_max does NOT change with R2. Only s_m changes. This is frequently tested.

Shortcut: If $s_m=R2/X2$: $T_{start}/T_{max} = 2*s_m / (1 + s_m^2)$. Quick ratio formula.

KEY: [THEORY-REPEATED] Starting methods: DOL (small motors), Star-Delta ($I_{st}=1/3$ of DOL), Autotransformer ($I_{st}=x^2$ times), Rotor resistance (slip-ring only).

KEY: [THEORY-REPEATED] Star-Delta starting: Starting current = 1/3 of DOL current. Starting torque = 1/3 of DOL torque. Cheap but limited.

KEY: [THEORY-REPEATED] Speed control: Pole changing (discrete speeds), V/f control (smooth, maintains flux), Rotor resistance (slip-ring only, lossy).

KEY: [THEORY] Cogging: motor refuses to start at certain rotor positions (slots = integral multiple of poles). Crawling: runs at 1/7th speed (7th harmonic torque).

KEY: [THEORY] Double cage: outer cage high-R low-X (starting), inner cage low-R high-X (running). Good starting torque without external resistance.

4.4 SYNCHRONOUS MACHINES

EMF of Alternator [FFF]

$$E_{ph} = 4.44 * K_w * f * \Phi * T_{ph}$$

$$K_w = K_p * K_d \text{ (winding factor)}$$

$$K_p = \cos(\alpha/2) \text{ [pitch factor, } \alpha = \text{short-pitch angle]}$$

$$K_d = \sin(m\beta/2) / (m\sin(\beta/2)) \text{ [distribution factor]}$$

$$\beta = 180/\text{slots_per_pole}, m = \text{slots/pole/phase}$$

Where: K_w =winding factor (0.9-0.96), K_p =pitch factor, K_d =distribution factor, T_{ph} =turns/phase.

Use when: Finding generated EMF of alternator/synchronous generator

Condition: Full pitch: $K_p=1$. Concentrated winding: $K_d=1$. Both reduce for practical machines.

Trap: K_p and K_d are always ≤ 1 . Total $K_w = K_p * K_d$ is always less than 1.

Shortcut: For full-pitch concentrated winding: $E = 4.44 * f * \Phi * T$ (same as transformer). K_w reduces this.

Voltage Regulation (Alternator) [FF]

$$VR\% = (E_f - V_t) / V_t \times 100$$

E_f = generated EMF at full load

V_t = terminal voltage

$$\text{Synchronous impedance method: } E_f = \sqrt{(V \cos(\phi) + I R_a)^2 + (V \sin(\phi) + I X_s)^2} \text{ [lagging]}$$

For leading: change + to - before $I X_s$ term

Where: E_f =full-load EMF, V_t =terminal voltage, X_s =synchronous reactance, R_a =armature resistance.

Use when: Finding voltage regulation of alternator

Condition: Lagging PF: VR is positive (high). Leading PF: VR can be negative.

Trap: Sign change for leading vs lagging (same trap as transformer regulation).

Shortcut: EMF method gives pessimistic (higher) regulation. MMF method gives optimistic (lower). ZPF/Potier is most accurate.

Power-Angle Equation [FFF]

$$P = (V E_f / X_s) \sin(\delta) \text{ [per phase]}$$

$$\text{Max power: } P_{max} = V E_f / X_s \text{ [at } \delta = 90^\circ \text{ deg]}$$

$$\text{Reactive power: } Q = (V / X_s) (E_f \cos(\delta) - V)$$

Where: δ =power/load angle, V =terminal voltage, E_f =excitation EMF, X_s =synchronous reactance.

Use when: Power transfer and stability analysis of synchronous machines

Condition: P_{max} at $\delta=90$. Beyond 90: unstable. Steady-state stability limit: $\delta < 90^\circ$.

Trap: Over-excited ($E_f > V$): supplies reactive power (leading PF, like capacitor). Under-excited: absorbs reactive power.

Shortcut: Synchronous condenser: synchronous motor at no-load used for PF correction (over-excited).

KEY: [THEORY-REPEATED] V-curves: I_a vs I_f at constant load. Minimum I_a at unity PF. Left=overexcited (leading), Right=underexcited (lagging).

KEY: [THEORY-REPEATED] Inverted V-curves: PF vs I_f . Maximum PF (unity) at middle. Over-excited=leading, Under-excited=lagging.

KEY: [THEORY-REPEATED] Synchronous motor starting: NOT self-starting. Methods: damper winding (most common), pony motor, VFD.

KEY: [THEORY] Hunting: oscillation of rotor about synchronous position. Damper winding provides damping torque to reduce hunting.

KEY: [THEORY] Synchronization conditions: Same voltage, same frequency, same phase sequence, same phase angle. Dark lamp / synchroscope methods.

5. POWER SYSTEMS

5.1 GENERATION & ECONOMICS

FACTOR	FORMULA	TYPICAL VALUE	NOTES
Load Factor	Avg demand / Max demand	0.5-0.7	Higher = better utilization
Demand Factor	Max demand / Connected load	<1 always	Not all loads ON at once
Diversity Factor	Sum indiv. max / System max	>1 always	Higher = cheaper per kW
Capacity Factor	Actual energy / (Capacity x T)	0.3-0.5	CF <= LF always
Utilization Factor	Max demand / Rated capacity	<=1	How much capacity used
Reserve Margin	(Installed - Peak) / Peak	15-20%	Safety margin
Plant Factor	Avg demand / Rated capacity		CF ≈ PF if no reserve

TRAP: Diversity Factor > 1 (always). All other factors <= 1. This is commonly tested.

TRAP: Load Factor = Average Load / Maximum Demand. NOT Average/Connected Load (that is utilization factor).

Economic Dispatch [FF]

Condition: $dF_1/dP_1 = dF_2/dP_2 = \dots = \lambda$ (incremental cost)

With losses: $(dF_i/dP_i) * 1/(1-dP_L/dP_i) = \lambda$

Penalty factor: $L_i = 1/(1-dP_L/dP_i)$

Where: F=fuel cost, P=power output, λ =incremental cost (Rs/MWh), P_L =transmission loss.

Use when: Optimal load sharing between generating units to minimize total fuel cost

Condition: Without losses: equal incremental cost. With losses: include penalty factors.

Trap: Penalty factor is always >= 1. Plant closer to load has lower penalty factor.

Shortcut: For two plants: if $IC_1=IC_2$ then they share load equally (without losses).

5.2 TRANSMISSION LINES

LINE TYPE	LENGTH	MODEL	ABCD PARAMETERS
Short	< 80 km	Series Z only	A=1, B=Z, C=0, D=1
Medium (Nominal pi)	80-250 km	Lumped Y/2 at each end	A=1+YZ/2, B=Z, C=Y(1+YZ/4), D=A
Medium (Nominal T)	80-250 km	Lumped Z/2+Y+Z/2	A=1+YZ/2, B=Z(1+YZ/4), C=Y, D=A
Long	> 250 km	Distributed params	A=cosh(gamma*l), B=Zc*sinh(gamma*l)

Short Line Model [FFF]

$$V_s = V_r + I_r * Z \quad (Z = R + jX)$$

$$I_s = I_r$$

$$VR\% = (|V_s| - |V_r|) / |V_r| \times 100$$

$$\text{Approx: } VR \approx I_r (R \cos(\phi) + X \sin(\phi)) / V_r \quad [\text{lagging}]$$

$$\text{Efficiency: } \eta = P_r / (P_r + 3 * I^2 * R) \times 100$$

Where: V_s =sending-end, V_r =receiving-end, Z =series impedance, I_r =load current.

Use when: Lines < 80 km. Most exam problems use short-line model.

Condition: Shunt capacitance ignored. Only series impedance considered.

Trap: VR formula sign: + for lagging (most common), - for leading.

Shortcut: For short line: ABCD: A=D=1, B=Z, C=0. Simplest model.

Surge Impedance & SIL [FF]

$$Z_c = \sqrt{L/C} = \sqrt{z/y} \quad (\text{surge/characteristic impedance})$$

$$SIL = V_L^2 / Z_c \quad (\text{Surge Impedance Loading, MW})$$

At SIL: voltage profile is flat, reactive power = 0

Where: Z_c in Ohm, V_L =line voltage (kV), SIL in MW.

Use when: Evaluating transmission line loading capability

Condition: At SIL: no reactive power flow, voltage constant along line. Below SIL: Ferranti effect possible.

Trap: SIL is not a limit but a reference. Lines can operate above or below SIL.

Shortcut: Typical Z_c : 400 Ohm (overhead), 40 Ohm (cable). SIL of 400kV line $\approx$ 500 MW.

Corona [FF]

$$\text{Critical Disruptive Voltage: } V_d = 21.21 * m_0 * \delta * r * \ln(D/r) \quad \text{kV (rms)}$$

$$\text{Visual Critical Voltage: } V_v = 21.21 * m_v * \delta * r * (1 + 0.3/\sqrt{\delta * r}) * \ln(D/r)$$

$$\text{Corona loss (Peek): } P = 242.2/\delta * (f+25) * \sqrt{r/D} * (V-V_d)^2 * 10^{-5} \quad \text{kW/km/phase}$$

Where: m_0 =surface irregularity factor, δ =air density, r =conductor radius (cm), D =spacing (cm).

Use when: Transmission line design, voltage selection

Condition: Corona increases with: higher voltage, rain/fog, smaller conductor, closer spacing.

Trap: Corona loss formula uses $(V-V_d)^2$. If $V < V_d$, no corona loss.

Shortcut: Factors increasing corona: high altitude (low δ), rough surface (low m_0), rain (m_v reduces).

KEY: [THEORY-REPEATED] Ferranti effect: receiving-end voltage > sending-end voltage at no-load or light load. Due to line capacitance charging.

KEY: [THEORY-REPEATED] ABCD parameter property: $AD - BC = 1$ always. For symmetrical network: $A = D$.

KEY: [THEORY] Bundle conductors: reduce corona, reduce reactance, increase capacitance, increase SIL.

KEY: [THEORY] Skin effect: AC current flows near conductor surface. Increases effective resistance. More pronounced at higher frequencies.

5.3 UNDERGROUND CABLES & INSULATORS

Cable Capacitance [FF]

$$C = 2\pi \epsilon_0 \epsilon_r / \ln(R/r) \text{ F/m}$$

$$\text{Charging current: } I_c = 2\pi f C V \text{ A/km}$$

Where: R=outer radius, r=inner conductor radius, ϵ_r =relative permittivity.

Use when: Cable design, charging current calculation

Condition: Maximum stress at conductor surface: $g_{\max} = V / (r \cdot \ln(R/r))$.

Trap: Stress is maximum at inner conductor (r), not outer sheath (R).

Shortcut: Capacitance grading: uses layers of different ϵ_r to equalize stress.

String Efficiency (Insulators) [FF]

$$\text{String efficiency} = V_{\text{total}} / (n \cdot V_{\text{across_bottom_disc}}) \times 100\%$$

Ideal: 100% (uniform voltage distribution)

Practical: 70-80% (non-uniform due to stray capacitance)

Where: n=number of discs, V_{total} =line voltage across string.

Use when: Insulator design, number of discs calculation

Condition: Bottom disc has highest voltage. Guard rings improve string efficiency.

Trap: String efficiency is always < 100% for suspension insulators (unless guard ring makes it 100%).

Shortcut: More discs = lower string efficiency (unless guard ring used). Counter-intuitive.

KEY: [THEORY-REPEATED] Types of insulators: Pin (up to 33kV), Suspension (above 33kV), Strain (at dead-end), Shackle (low voltage).

5.4 PER-UNIT SYSTEM

Per-Unit Definitions & Base Conversion [FFF]

p.u. value = Actual value / Base value

Base power: S_{base} (chosen, same throughout)

Base voltage: V_{base} (different at each voltage level, transformer ratio)

Base current: $I_{base} = S_{base} / (\sqrt{3} * V_{base})$

Base impedance: $Z_{base} = V_{base}^2 / S_{base} = V_{base} / (\sqrt{3} * I_{base})$

Base conversion: $Z_{pu_new} = Z_{pu_old} * (S_{base_new}/S_{base_old}) * (V_{base_old}/V_{base_new})^2$

Where: All in consistent units (MVA, kV, kA, Ohm).

Use when: All power system analysis, fault calculations

Condition: S_{base} is SAME throughout system. V_{base} changes at each transformer according to turns ratio.

Trap: Z_{base} changes with $(V_{base})^2/S_{base}$ at each level. Impedances must be on SAME base for addition.

Shortcut: Transformer impedance is SAME in p.u. on both sides (key advantage of p.u. system).

5.5 SYMMETRICAL COMPONENTS & FAULT ANALYSIS

Symmetrical Components [FFF]

$V_a = V_0 + V_1 + V_2$

$V_b = V_0 + a^2 * V_1 + a * V_2$

$V_c = V_0 + a * V_1 + a^2 * V_2$

where $a = 1 \angle(120) = -0.5 + j0.866$

Inverse: $V_0 = (V_a + V_b + V_c)/3$

$V_1 = (V_a + a * V_b + a^2 * V_c)/3$

$V_2 = (V_a + a^2 * V_b + a * V_c)/3$

Where: V_0 =zero sequence, V_1 =positive, V_2 =negative. $a=1 \angle(120)$.

Use when: Unbalanced fault analysis

Condition: $a^2 = 1 \angle(240) = -0.5 - j0.866$. $a^3 = 1$. $1 + a + a^2 = 0$.

Trap: Sign of exponent in a . $a^2 = 1 \angle(240)$, NOT $\angle(120)$.

Shortcut: For balanced 3-phase: only positive sequence exists. $V_0=0$, $V_2=0$.

FAULT TYPE	FAULT CURRENT I_f	SEQUENCE CONNECTION	SEVERITY RANK
3-phase (LLL)	V_f / Z_1	Only Z_1	2nd or 3rd
LG (SLG)	$3 * V_f / (Z_0 + Z_1 + Z_2)$	$Z_0 + Z_1 + Z_2$ in series	Usually most severe
LL (Line-Line)	$\sqrt{3} * V_f / (Z_1 + Z_2)$	$Z_1 + Z_2$ in series	Least severe
LLG	$3 * V_f / (Z_1 + Z_0 Z_2)$	$Z_1 + Z_0 Z_2$	2nd most severe

TRAP: Fault severity (typical): LG > LLG > 3-phase > LL. But 3-phase is most severe in terms of MVA for circuit breaker rating.

TRAP: For 3-phase fault: only Z_1 used. For LG: $Z_0 + Z_1 + Z_2$ in SERIES. For LL: $Z_1 + Z_2$ only (no Z_0).

KEY: Fault MVA = $V_{base}^2 / Z_{fault} = S_{base} / Z_{pu_fault}$.

5.6 PROTECTION SYSTEMS

IDMT Relay (Inverse Definite Minimum Time) [FFF]

Operating time: $t = (k * TMS) / (PSM^n - 1)$

IEC Standard Inverse: $k=0.14$, $n=0.02$

Very Inverse: $k=13.5$, $n=1$

Extremely Inverse: $k=80$, $n=2$

$PSM = I_{\text{fault}} / I_{\text{setting}}$

Plug Setting (PS): $I_{\text{setting}} = PS \times CT_{\text{secondary_rating}}$

Where: TMS=time multiplier setting, PSM=plug setting multiplier, PS=plug setting (fraction of CT rating).

Use when: Overcurrent protection of feeders and equipment

Condition: Higher PSM = lower operating time (faster tripping for larger faults).

Trap: PSM uses relay coil current, not primary current. Must account for CT ratio.

Shortcut: For coordination: upstream relay has higher TMS than downstream.

Differential Protection [FF]

Operating current: $I_{\text{op}} = |I_1 - I_2|$

Restraining current: $I_{\text{res}} = (|I_1| + |I_2|) / 2$

Relay operates when: $I_{\text{op}} > k \cdot I_{\text{res}} + I_{\text{min}}$

k = slope (typically 15-40%)

Where: I_1 =primary CT current, I_2 =secondary CT current (both referred to same side).

Use when: Transformer, generator, busbar protection

Condition: Must match CT ratios on both sides. Mismatch causes false differential current.

Trap: Through-fault current should produce zero differential. Mismatch causes maloperation.

Shortcut: Percentage differential relay: slope k provides restraint against CT errors and tap-changing.

Distance Relay Types [FF]

Impedance relay: $|Z| = |V/I| < Z_{\text{set}}$ (circular, centered at origin)

Reactance relay: $X = \text{Im}(V/I) < X_{\text{set}}$ (horizontal line)

Mho relay: $|Z - Z_{\text{set}}/2| < Z_{\text{set}}/2$ (circular, passes through origin)

Admittance relay: same as Mho (different perspective)

Where: Z =measured impedance, V =relay voltage, I =relay current.

Use when: Transmission line protection (zones of protection)

Condition: Zone 1: 80-85% of line (instantaneous). Zone 2: 120% (time delay). Zone 3: backup (longer delay).

Trap: Mho relay is directional and most used. Impedance relay is non-directional.

Shortcut: Reactance relay: unaffected by arc resistance (best for short lines). Mho: unaffected by load encroachment.

KEY: [THEORY-REPEATED] Buchholz relay: gas-actuated, for oil-filled transformers. Float for minor faults (alarm), baffle for major faults (trip).

KEY: [THEORY-REPEATED] Circuit breaker making current = $2.55 \times I_{\text{sc_rms}}$ (accounts for DC offset). Breaking current = $I_{\text{sc_rms}}$.

KEY: [THEORY] RRRV = Rate of Rise of Recovery Voltage. Higher RRRV = more difficult to interrupt. $RRRV = V_{\text{peak}} / (t_{\text{recovery}})$.

KEY: [THEORY] Current chopping: premature interruption of small inductive currents. Causes high voltage transients ($L \cdot di/dt$).

KEY: [THEORY-REPEATED] Neutral grounding: Solid (high fault current, low overvoltage), Resistance (limited fault current), Reactance, Peterson coil (resonant, cancels I_c).

5.7 POWER SYSTEM STABILITY

Swing Equation [FF]

$$M \cdot \frac{d^2\delta}{dt^2} = P_m - P_e = P_a$$

$M = H / (\pi \cdot f_0)$ [inertia constant in MJ-s/elec-rad]

$H = \text{stored kinetic energy} / \text{machine rating (MJ/MVA)}$

$$P_e = P_{\max} \cdot \sin(\delta) \text{ [power-angle equation]}$$

Where: M =inertia, δ =rotor angle, P_m =mechanical input, P_e =electrical output, P_a =accelerating power.

Use when: Transient stability analysis

Condition: If $P_m > P_e$: rotor accelerates (δ increases). If $P_m < P_e$: decelerates.

Trap: H is in MJ/MVA (per unit). Typical H : 2-9 for generators. Higher H = more stable.

Shortcut: Swing equation is the fundamental equation for ALL stability analysis.

Equal Area Criterion [FF]

Stability condition: Accelerating area $A_1 \leq$ Decelerating area A_2

$A_1 = \text{integral from } \delta_{\theta} \text{ to } \delta_{cl} \text{ of } (P_m - P_e) d(\delta)$

$A_2 = \text{integral from } \delta_{cl} \text{ to } \delta_{\max} \text{ of } (P_e - P_m) d(\delta)$

Critical clearing angle: $\cos(\delta_{cr}) = (\pi - 2\delta_{\theta}) \sin(\delta_{\theta}) - \cos(\delta_{\theta})$ [simple case]

For fault with $P_e \text{ during} = 0$: $\cos(\delta_{cr}) = (P_m/P_{\max}) \cdot (\pi - 2\delta_{\theta}) + \cos(\delta_{\theta})$

Where: A_1 =accelerating area, A_2 =decelerating area, δ_{cr} =critical clearing angle.

Use when: Determining transient stability limit, critical clearing angle/time

Condition: System is stable if $A_2 \geq A_1$. Maximum swing angle where $A_1 = A_2$ is the limit.

Trap: Equal area criterion only works for ONE machine vs infinite bus. Not for multi-machine.

Shortcut: Higher inertia H = more time to clear fault = higher CCT (critical clearing time).

KEY: [THEORY-REPEATED] Steady-state stability limit: $P_{\max} = E \cdot V / X_s$. Increase E (excitation) or decrease X_s to improve.

KEY: [THEORY] Methods to improve transient stability: faster fault clearing, higher inertia, lower reactance, series capacitors, HVDC, braking resistors.

6. CONTROL SYSTEMS

6.1 TRANSFER FUNCTION & BLOCK DIAGRAM

Closed-Loop Transfer Function [FFF]

$$T(s) = G(s) / (1 + G(s) \cdot H(s)) \text{ [negative feedback]}$$

$$T(s) = G(s) / (1 - G(s) \cdot H(s)) \text{ [positive feedback]}$$

$$\text{Characteristic equation: } 1 + G(s) \cdot H(s) = 0$$

Where: $G(s)$ =forward path TF, $H(s)$ =feedback TF, $T(s)$ =closed-loop TF.

Use when: All closed-loop system analysis

Condition: Negative feedback (most common): denominator is $1+GH$. Positive: $1-GH$.

Trap: Confusing sign: negative feedback has + in denominator, positive has -.

Shortcut: For unity feedback: $H(s)=1$, $T(s) = G(s)/(1+G(s))$.

Mason's Gain Formula [FF]

$$T = \frac{\sum (P_k \cdot \Delta_k)}{\Delta}$$

$$\Delta = 1 - \sum (L_i) + \sum (L_i \cdot L_j \text{ non-touching}) - \sum (L_i \cdot L_j \cdot L_k) + \dots$$

P_k = k-th forward path gain

Δ_k = cofactor of k-th path (Δ with all touching loops removed)

Where: L_i =individual loop gains, P_k =forward path gains.

Use when: Signal flow graphs (faster than block diagram reduction for complex systems)

Condition: Non-touching loops: loops that share no common node.

Trap: Forgetting to remove touching loops when computing Δ_k (cofactor).

Shortcut: For simple systems with 1 forward path and 1 loop: $T = P/(1-L)$.

6.2 STEADY-STATE ERROR

SYSTEM TYPE	$K_p = \lim_{s \rightarrow 0} G(s)$	$K_v = \lim_{s \rightarrow 0} sG(s)$	$K_a = \lim_{s \rightarrow 0} s^2G(s)$	$\lim_{s \rightarrow 0} G(s)$ (step)	$e_{ss}(\text{ramp})$	$e_{ss}(\text{parabola})$
Type 0	K (finite)	0	0	$1/(1+K)$	infinity	infinity

SYSTEM TYPE	$K_p = \lim_{s \rightarrow 0} G(s)$	$K_v = \lim_{s \rightarrow 0} sG(s)$	$K_a = \lim_{s \rightarrow 0} s^2 G(s)$	$e_{ss}(\text{step})$	$e_{ss}(\text{ramp})$	$e_{ss}(\text{parabola})$
Type 1	infinity	K (finite)	0	0	1/K	infinity
Type 2	infinity	infinity	K (finite)	0	0	1/K

TRAP: System TYPE = number of pure integrators (1/s factors) in open-loop $G(s)H(s)$. System ORDER = highest power of s in denominator.

TRAP: Type 0 has finite error for step. Type 1 has zero error for step but finite for ramp. Type 2 has zero for step and ramp.

KEY: $e_{ss} = R(s) / (1 + G(s)H(s))$ evaluated using Final Value Theorem: $\lim_{s \rightarrow 0} sE(s)$.

6.3 STABILITY ANALYSIS

Routh-Hurwitz Criterion [FFF]

For char. eq: $a_n s^n + a_{n-1} s^{n-1} + \dots + a_0 = 0$

Form Routh array. First column sign changes = RHP roots.

Necessary conditions: all coefficients present and same sign.

Special cases: zero in first column (replace with epsilon), entire row zero (auxiliary equation).

Where: Determines stability without solving characteristic equation.

Use when: Checking if closed-loop system is stable (all roots in LHP)

Condition: Necessary condition: all coefficients positive (for stability). Sufficient: also no sign changes in 1st column.

Trap: If ANY coefficient is zero or negative: system is UNSTABLE (quick check before building full array).

Shortcut: Row of zeros: use auxiliary equation from row above. Differentiate and replace zero row.

Bode Plot - Gain/Phase Margins [FFF]

Gain crossover freq (ω_{gc}): $|G(j\omega_{gc})| = 1$ (0 dB)

Phase crossover freq (ω_{pc}): $\angle G(j\omega_{pc}) = -180^\circ$

Gain Margin: $GM = -20 \log |G(j\omega_{pc})|$ dB [evaluated AT phase crossover]

Phase Margin: $PM = 180 + \angle G(j\omega_{gc})$ [evaluated AT gain crossover]

Stability: $GM > 0$ AND $PM > 0$

Where: GM in dB, PM in degrees. Both must be positive for stability.

Use when: Frequency-domain stability analysis

Condition: GM measured at phase crossover (where phase = -180). PM measured at gain crossover (where gain = 0 dB).

Trap: GM and PM measured at DIFFERENT frequencies. Most common confusion: measuring both at same frequency.

Shortcut: Typical design: $GM \geq 6$ dB, $PM \geq 30$ -60 deg.

6.4 ROOT LOCUS

Root Locus Rules [FFF]

1. # branches = # OL poles (n)

2. Start at OL poles ($K=0$), end at OL zeros ($K=\infty$) or infinity

3. On real axis: locus exists to LEFT of odd number of real poles+zeros

4. # Asymptotes = $n - m$ (poles minus zeros)

5. Asymptote angles = $(2k+1) \cdot 180 / (n-m)$, $k=0, 1, \dots, (n-m-1)$

6. Centroid = $(\text{Sum of poles} - \text{Sum of zeros}) / (n - m)$

7. Breakaway: $dK/ds = 0$ on real axis between poles

8. Angle of departure from complex pole: $180 - (\text{sum of angles from other poles}) + (\text{sum of angles from zeros})$

9. Imaginary axis crossing: use Routh array with K as variable

Where: n =number of open-loop poles, m =number of open-loop zeros.

Use when: Sketching root locus for gain variation, finding stability limits

Condition: Locus on real axis: count poles AND zeros to the RIGHT. If odd count, locus exists there.

Trap: Asymptote formula: $(2k+1) \cdot 180$, NOT $2k \cdot 180$. Common error in angle calculation.

Shortcut: Centroid and angles fully determine asymptotic behavior. Sketch asymptotes first.

6.5 COMPENSATORS

COMPENSATOR	TF FORM	EFFECT	WHEN TO USE
Lag	$(1+T_1s)/(1+aT_1s)$, $a>1$	Improves SS accuracy, reduces BW	Need lower ess, PM OK

COMPENSATOR	TF FORM	EFFECT	WHEN TO USE
Lead	$(1+T_2s)/(1+bT_2s)$, $b<1$	Improves transient, increases BW	Need more PM/speed
Lead-Lag	Combination	Both improvements	Need both SS and transient
PID	$K_p + K_i/s + K_d*s$	Complete control	General purpose industrial

KEY: [THEORY-REPEATED] PID: P=reduces error, I=eliminates SS error, D=improves transient response. Most widely used industrial controller.

7. UTILIZATION (HEATING, WELDING, TRACTION)

7.1 ELECTRIC HEATING

Resistance Heating [FF]

$$H = I^2 \cdot R \cdot t \text{ Joules} = V^2 \cdot t / R$$

For oven: $\theta(t) = \theta_f \cdot (1 - e^{-t/T})$ [heating]

$\theta(t) = \theta_i \cdot e^{-t/T}$ [cooling]

$T = \text{thermal time constant} = \text{Heat capacity} / \text{Heat dissipation rate}$

Where: H =heat (J), θ_f =final temp rise, T =thermal time constant.

Use when: Resistance ovens, room heaters, water heaters

Condition: Heating curve is exponential rise. Cooling is exponential decay.

Trap: Temperature rises to 63.2% of final in one time constant (same as electrical RC).

Shortcut: Power = V^2/R . To double heating rate, double voltage (quadruples power).

Induction Heating [FF]

$$P = K \cdot f \cdot B_{\max}^2 \cdot t^2 \text{ (eddy current loss in workpiece)}$$

$f = 50 \text{ Hz to } 500 \text{ kHz}$ depending on application

Where: P =power, f =frequency, $B_{\max}$ =flux density, t =thickness of workpiece.

Use when: Hardening, melting, brazing of conducting materials

Condition: Higher frequency: heating concentrated near surface (skin effect). Used for surface hardening.

Trap: Induction heating is for CONDUCTORS only. Non-conductors use dielectric heating.

Shortcut: Low frequency (50Hz): deep penetration. High frequency (MHz): surface only.

Dielectric Heating [FF]

$$P = 2\pi \cdot f \cdot C \cdot V^2 \cdot \tan(\delta) = 5.56 \times 10^{-11} \cdot f \cdot E^2 \cdot \epsilon_r \cdot \tan(\delta) \cdot \text{Volume } W$$

Where: f =frequency (Hz), ϵ_r =relative permittivity, $\tan(\delta)$ =loss tangent, E =electric field.

Use when: Heating non-conductors (wood, plastic, food, ceramics)

Condition: Frequency: typically 10-50 MHz. Material must have high loss tangent.

Trap: Dielectric heating for NON-conductors. Induction heating for CONDUCTORS.

Shortcut: Microwave oven: 2.45 GHz dielectric heating. Used for food processing.

7.2 ELECTRIC WELDING

Welding Energy [F]

$$H = I^2 \cdot R \cdot t \text{ Joules (resistance welding)}$$

For spot welding: $H = I^2 \cdot R \cdot t \cdot \text{cycles/sec}$

Arc welding: $P = V_{\text{arc}} \cdot I_{\text{arc}}$ Watts

Where: I =welding current, R =contact resistance, t =time.

Use when: Spot, seam, butt welding calculations

Condition: Spot welding: brief high current pulse. Seam: continuous rolling. Butt: entire cross-section.

Trap: Heat is proportional to I^2 , not I . Doubling current quadruples heat.

Shortcut: For AC welding: use RMS values of current and voltage.

7.3 ELECTRIC TRACTION

Tractive Effort & Speed-Time [FF]

$$F_t = M \cdot a + M \cdot g \cdot \sin(\theta) + r \text{ [total tractive effort, N]}$$

where: $M \cdot a$ = accelerating force, $M \cdot g \cdot \sin(\theta)$ = gravity component, r = train resistance

Specific energy consumption: $E_{\text{sp}} = \text{Total energy} / (\text{Mass} \times \text{Distance})$ Wh/tonne-km

Average speed: $V_a = \text{Distance} / \text{Running time}$

Schedule speed: $V_s = \text{Distance} / (\text{Running time} + \text{Stop time})$

Dead weight: $W_d = \text{Weight of train without payload}$

Accelerating weight: $W_e = 1.1 \cdot W_d$ (accounts for rotational inertia, approx 10% addition)

Where: F_t =tractive effort (N), M =mass (kg), a =acceleration (m/s^2), θ =gradient angle.

Use when: Train movement, energy consumption, speed calculations

Condition: Schedule speed < Average speed (includes stop time). Distinguish carefully.

Trap: Forgetting to include gradient and resistance components in tractive effort.

Shortcut: For level track: $F_t = M \cdot a + r$. Gradient adds $M \cdot g \cdot \sin(\theta) = M \cdot g \cdot G/100$ ($G = \% \text{ gradient}$).

KEY: [THEORY-REPEATED] Speed-time curve phases: Acceleration -> Free-running (constant speed) -> Coasting (power off) -> Braking.

KEY: [THEORY-REPEATED] Regenerative braking: motor acts as generator, returns energy to supply. Energy saving 10-30%.

KEY: [THEORY] Traction motors: DC series (traditional), AC induction (modern, V/f or vector control).

KEY: [THEORY] Co-efficient of adhesion = Tractive effort / Weight on driving wheels. Typically 0.2-0.3 for dry rail.

8. MEASUREMENTS & INSTRUMENTATION

8.1 MEASUREMENT BRIDGES - COMPLETE FORMULAS

BRIDGE	MEASURES	BALANCE CONDITION	KEY NOTES
Wheatstone	R (medium)	$R_1 \cdot R_3 = R_2 \cdot R_x \Rightarrow R_x = R_2 \cdot R_3 / R_1$	DC bridge, most basic
Kelvin Double	R (very low)	Eliminates lead resistance	For $R < 1 \text{ Ohm}$
Maxwell Inductance	L, R of coil	$L_x = R_2 \cdot R_3 \cdot C_1$, $R_x = R_2 \cdot R_3 / R_1$	Low Q coils ($1 < Q < 10$)
Maxwell Wien	L using C std	$L_x = C \cdot R_2 \cdot R_3$, $R_x = R_2 \cdot R_3 / R_1$	Same as above, C based
Hay Bridge	L (high R)	$L_x = R_2 \cdot R_3 \cdot C_1 / (1 + \omega^2 \cdot R_1^2 \cdot C_1^2)$	Q > 10, frequency dependent
Anderson	L using C	Modified Maxwell, more flexible	Fixed C, variable R
Schering	C, tan(delta)	$C_x = C_s \cdot R_3 / R_1$, $\tan(d) = \omega \cdot C_1 \cdot R_1$	HV cable/insulation test
Wien	Frequency	$f = 1 / (2 \cdot \pi \cdot R \cdot C)$ if $R_1 = R_2, C_1 = C_2$	Audio frequency measurement
De Sauty	C (comparison)	$C_x = C_s \cdot R_2 / R_1$	Simple capacitance comparison

TRAP: Maxwell bridge: for LOW Q coils. Hay bridge: for HIGH Q coils. Reversed in many MCQs.

TRAP: Schering bridge: used for HIGH VOLTAGE insulation testing. Loss tangent $\tan(\delta) = \omega \cdot C_1 \cdot R_1$.

KEY: Wien bridge: frequency measurement AND oscillator circuit. Balance at $f = 1 / (2 \cdot \pi \cdot R \cdot C)$.

8.2 INSTRUMENTS - CHARACTERISTICS

INSTRUMENT	PRINCIPLE	DEFLECTION proportional to	AC/DC	SCALE
PMMC	Permanent magnet + coil	I (current)	DC only	Uniform (linear)
Moving Iron	Attraction/Repulsion	I_{rms}	AC + DC	Non-uniform
Electrodynamometer	Two coils interaction	$I_1 \cdot I_2 \cdot \cos(\phi)$	AC + DC	Non-uniform
Induction type	Rotating magnetic field	Power (energy meter)	AC only	Uniform
Rectifier type	PMMC + rectifier	Average value	AC (calibrated RMS)	Uniform

TRAP: PMMC reads AVERAGE (for AC, reads zero). Moving Iron reads TRUE RMS. Rectifier type reads average but calibrated for RMS (assumes sine).

TRAP: If non-sinusoidal waveform measured by rectifier instrument: multiply reading by actual Form Factor / 1.11.

8.3 ERRORS & SENSITIVITY

Instrument Errors [FF]

Absolute error = Measured - True

Relative error = (Measured - True) / True x 100%

% error = (Absolute error / FSD) x 100% [for accuracy class]

Limiting error = Accuracy class x FSD / Reading x 100%

Where: FSD = full scale deflection.

Use when: Error analysis in measurements

Condition: Error is expressed as % of FSD for accuracy class. Actual % error increases at lower readings.

Trap: A 1% accuracy instrument reading at 10% of FSD has 10% ACTUAL error. Always read near FSD.

Shortcut: Best accuracy: take readings in upper 2/3 of scale.

8.4 CRO, Q-METER, DIGITAL

CRO (Cathode Ray Oscilloscope)

Time period: $T = (\text{No. of divisions}) \times (\text{Time/div setting})$

Frequency: $f = 1/T$

Amplitude: $V_{pp} = (\text{No. of divisions}) \times (\text{Volt/div setting})$

Phase measurement: $\phi = (d/D) \times 360 \text{ deg}$, d =horizontal shift, D =full cycle width

Lissajous figures: $f_y/f_x = \text{tangencies_on_horizontal} / \text{tangencies_on_vertical}$

Q-Meter

$$Q = X_L/R = 1/(w \cdot C \cdot R) = w \cdot L/R \text{ (at resonance)}$$

Measures Q-factor by series resonance method. Adjust C for resonance, read V_C .

$$Q = V_C / V_{\text{source}} \text{ (voltage magnification at resonance)}.$$

Digital Instruments

$$\text{Resolution of n-bit ADC: } V_{\text{LSB}} = V_{\text{ref}} / 2^n$$

DVM resolution: 1/counts. 3.5 digit DVM: 0-1999 counts, resolution = 0.05%

Quantization error: $\pm V_{\text{LSB}}/2$ (maximum).

KEY: [THEORY-REPEATED] 3.5 digit DVM: max reading 1999. 4.5 digit: max 19999. Resolution = $1/\text{max_count}$.

9. ANALOG & DIGITAL ELECTRONICS

9.1 DIODES & RECTIFIERS

PARAMETER	HALF-WAVE	FULL-WAVE (CT)	FULL-WAVE BRIDGE
V _{dc}	$V_m/\pi = 0.318V_m$	$2V_m/\pi = 0.636V_m$	$2V_m/\pi = 0.636V_m$
V _{rms}	$V_m/2 = 0.5V_m$	$V_m/\sqrt{2} = 0.707V_m$	$V_m/\sqrt{2} = 0.707V_m$
Ripple factor	1.21	0.482	0.482
Efficiency	40.6%	81.2%	81.2%
PIV	V_m	$2V_m$	V_m
TUF	0.287	0.693	0.812
Ripple freq	f	2f	2f
No. of diodes	1	2	4

TRAP: PIV of bridge rectifier = V_m (NOT $2V_m$). PIV of center-tap = $2V_m$. Commonly swapped in MCQs.

TRAP: Ripple factor of half-wave = 1.21 (>1, more AC than DC). Full-wave = 0.482 (<1, more DC).

Diode equation: $I = I_s * (e^{V/(n*V_T)} - 1)$, $V_T = kT/q = 26\text{mV}$ at 27C. $n=1$ for Ge, $n=2$ for Si.

KEY: Zener regulator: $V_{out} = V_Z$ (constant). I_Z must be $> I_{Z_min}$ for regulation.

9.2 TRANSISTORS (BJT & FET)

CONFIG	CURRENT GAIN	VOLTAGE GAIN	Z _{in}	Z _{out}	PHASE
CE	beta (50-200)	Medium-High	Medium	Medium	180 deg
CB	alpha (<1)	High	Low	High	0 deg
CC (EF)	beta+1	~1 (unity)	Very High	Very Low	0 deg

$\alpha = I_C/I_E = \text{beta}/(1+\text{beta})$ | $\text{beta} = I_C/I_B = \alpha/(1-\alpha)$ | $I_E = I_B + I_C$

Transconductance: $g_m = I_C/V_T = 40*I_C$ (mA) mS. $r_e = V_T/I_E = 26/I_E$ (mA) Ohm.

Stability factor: $S = dI_C/dI_{C0}$. Smaller S = better stability. Voltage divider bias: best stability.

FET (JFET / MOSFET)

JFET Shockley equation: $I_D = I_{DSS} * (1 - V_{GS}/V_P)^2$

Transconductance: $g_m = g_{m0} * (1 - V_{GS}/V_P) = 2*I_{DSS}/|V_P| * (1 - V_{GS}/V_P)$

MOSFET (enhancement): $I_D = K*(V_{GS} - V_T)^2$, $K = \mu*C_{ox}*W/(2L)$

Voltage gain: $A_v = -g_m * R_D$ (common source). MOSFET: extremely high Z_{in} (10^{12} Ohm).

9.3 OP-AMP & DIGITAL LOGIC (Brief)

Inverting amp: $V_{out} = -(R_f/R_{in})*V_{in}$ | Non-inverting: $V_{out} = (1+R_f/R_{in})*V_{in}$

Summing amplifier: $V_{out} = -R_f*(V_1/R_1 + V_2/R_2 + \dots)$ | Diff amp: $V_{out} = (R_f/R_{in})*(V_2-V_1)$

Integrator: $V_{out} = -(1/RC)*\text{integral}(V_{in} dt)$ | Differentiator: $V_{out} = -RC*dV_{in}/dt$

GATE	EXPRESSION	TRUTH TABLE (2-input)	UNIVERSAL?
AND	$Y = A.B$	0,0,0,1	No
OR	$Y = A+B$	0,1,1,1	No
NOT	$Y = A'$	1,0 (1 input)	No
NAND	$Y = (A.B)'$	1,1,1,0	YES
NOR	$Y = (A+B)'$	1,0,0,0	YES
XOR	$Y = A \text{ xor } B$	0,1,1,0	No
XNOR	$Y = (A \text{ xor } B)'$	1,0,0,1	No

KEY: Boolean: $A+A'=1$, $A.A'=0$, $A+AB=A$, $A(A+B)=A$. De Morgan: $(AB)'=A'+B'$, $(A+B)'=A'.B'$.

KEY: Flip-flops: SR (basic), JK (no forbidden state), D (data latch), T (toggle). JK is most versatile.

KEY: [THEORY] Number conversions: Binary to Decimal, Octal, Hex. BCD: each decimal digit = 4 bits. Gray code: adjacent codes differ by 1 bit.

KEY: ADC types: Flash (fastest), SAR (common), Dual-slope (most accurate). DAC: R-2R ladder, weighted resistor.

10. POWER ELECTRONICS & DRIVES

10.1 THYRISTOR FAMILY

DEVICE	TURN-ON	TURN-OFF	SWITCHING SPEED	TYPICAL USE
SCR	Gate pulse	Natural commutation	Slowest (ms)	AC-DC rectifiers, AC controllers
GTO	Gate pulse	Negative gate pulse	Medium	Choppers, inverters
TRIAC	Gate pulse (both dir)	Current zero	Slow	AC voltage controllers, dimmers
MOSFET	Gate voltage	Gate voltage	Very fast (ns)	High-freq DC-DC, switching
IGBT	Gate voltage	Gate voltage	Fast (us)	Medium freq, motor drives

TRAP: SCR latching current $I_L >$ holding current I_H . I_L needed to turn ON, I_H needed to stay ON. $I_L > I_H$ always.

KEY: [THEORY-REPEATED] SCR commutation: Natural (AC zero crossing), Forced (LC circuit, auxiliary SCR). Class A, B, C, D, E, F.

10.2 CONTROLLED RECTIFIERS

RECTIFIER TYPE	V _{dc} OUTPUT	CONDITION
1-ph Half-wave (R load)	$V_m(1+\cos a)/(2\pi)$	a =firing angle
1-ph Full-wave (R load)	$V_m(1+\cos a)/\pi$	a =firing angle
1-ph Full bridge (RL)	$2V_m\cos(a)/\pi$	Continuous conduction
3-ph Half-wave	$3\sqrt{3}V_m\cos(a)/(2\pi)$	a =firing angle
3-ph Full bridge	$3\sqrt{3}V_m\cos(a)/\pi$	Most common industrial

For continuous conduction (RL load): $V_{dc} = 2V_m\cos(a)/\pi$ [1-phase bridge]

Inversion mode: $a > 90^\circ$ deg, V_{dc} becomes negative (power flows back to AC supply).

TRAP: V_{dc} reduces as α increases. At $\alpha=90^\circ$: $V_{dc}=0$. At $\alpha>90^\circ$: V_{dc} negative (inversion).

10.3 DC-DC CHOPPERS

CHOPPER	V _{out}	CONDITION	ALSO CALLED
Step-down (Buck)	$D \cdot V_{in}$	$D = T_{on}/T$, $0 < D < 1$	Type A, Class A
Step-up (Boost)	$V_{in}/(1-D)$	$D = T_{on}/T$	Type B, Class B
Buck-Boost	$-D \cdot V_{in}/(1-D)$	Output inverted	Type C
Cuk	$-D \cdot V_{in}/(1-D)$	Capacitor coupled	Inverted output

KEY: D = duty cycle = $T_{on}/(T_{on}+T_{off})$. Varying D controls output voltage continuously.

10.4 INVERTERS

Single-phase inverter: Square wave output contains harmonics 1,3,5,7...

$V_1(\text{fundamental RMS}) = 4 \cdot V_{dc}/(\sqrt{2} \cdot \pi) = 0.9 \cdot V_{dc}$ [square wave]

PWM inverter: varies pulse width to control V_{out} and reduce harmonics.

3-phase inverter: 120 deg conduction or 180 deg conduction mode.

KEY: [THEORY] V/f control: maintains constant flux in induction motor. Below base speed: reduce V proportionally with f . Above base speed: V constant, f increases (field weakening).

KEY: [THEORY-REPEATED] 4-quadrant operation: Forward motoring, Forward braking, Reverse motoring, Reverse braking. Dual converter or H-bridge.

11. QUANTITATIVE APTITUDE - ALL FORMULAS

TOPIC	KEY FORMULAS	SHORTCUT
Percentage	$x\%$ of $A = xA/100$. %change = $(\text{new-old})/\text{old} \times 100$. Increase then $x\%$ decrease: net = $-x^2/100$ % loss	
Profit & Loss	Profit% = $(\text{SP}-\text{CP})/\text{CP} \times 100$. SP = $\text{CP}(1+\text{P}/100)$. Discount: SP = $\text{MP}(1-\text{d}/100)$. Two successive d_1, d_2 : $\text{d} = \text{d}_1 + \text{d}_2 - \text{d}_1 \times \text{d}_2 / 100$	
Simple Interest	SI = $\text{PRT}/100$. Amount $A = P + \text{SI}$	SI doubles in $T=100/R$ years
Compound Int.	$A = P(1+R/100)^n$. CI = $A - P$	Rule of 72: doubles in $72/R$ years (approx)
Ratio & Proportion	$a:b = c:d$ means $ad = bc$	Componendo-Dividendo: $(a+b)/(a-b) = (c+d)/(c-d)$
Average	Avg = Sum/n . Weighted avg = $\text{Sum}(w_i \times x_i) / \text{Sum}(w_i)$	If equal groups: avg of avgs = total avg
Time & Work	If A does in a days, rate = $1/a$ per day	A and B together: $1/a + 1/b = 1/T \Rightarrow T = ab/(a+b)$
Time & Distance	$D = S \times T$. Avg speed = $\text{Total } D / \text{Total } T$	Two equal distances at S_1, S_2 : Avg = $2 \times S_1 \times S_2 / (S_1 + S_2)$
Trains	Time to pass pole = L/S . To pass platform = $(L+P)/S$	Relative speed: same dir = $S_1 - S_2$, opposite = $S_1 + S_2$
Pipes & Cisterns	Fill rate = $1/T$. Two pipes: $1/A + 1/B = 1/T$	Leak: $1/A - 1/B = 1/T$ (fill - drain)
Permutation	$nPr = n!/(n-r)!$	With repetition: n^r
Combination	$nCr = n!/[r!(n-r)!]$	$nCr = nC(n-r)$. $nC0 = nCn = 1$
Probability	$P(E) = \text{favorable}/\text{total}$. $0 \leq P \leq 1$	$P(A \text{ or } B) = P(A) + P(B) - P(A \text{ and } B)$
Mensuration	Circle: $A = \pi r^2$, $C = 2\pi r$ Sphere: $V = 4\pi r^3/3$, $SA = 4\pi r^2$	
	Rectangle: $A = l \times b$, $P = 2(l+b)$	Cylinder: $V = \pi r^2 h$, $TSA = 2\pi r(r+h)$
	Triangle: $A = \sqrt{s(s-a)(s-b)(s-c)}$, $s = (a+b+c)/2$	Cone: $V = \pi r^2 h/3$, $CSA = \pi r l$
Number System	Divisibility: by 2 (last digit even), 3 (digit sum/3)	By 4: last 2 digits div by 4. By 8: last 3 digits.
Ages	Set up linear equations. Present= x , after n yrs= $x+n$	Usually 2 equations, 2 unknowns
Mixture/Alligation	Alligation: $(\text{d}_2 - \text{d}_{\text{mean}})/(\text{d}_{\text{mean}} - \text{d}_1) = n_1/n_2$	Quick ratio of two mixtures

12. REASONING SHORTCUTS

- * Analogies: Identify relationship (synonyms, antonyms, part-whole, tool-function, degree).
- * Classification: Find odd one out based on category (living/non-living, shape, number property).
- * Series completion: Number (+2,x2,+3...), Letter (A+2=C, +3=F...), Alpha-numeric patterns.
- * Coding-Decoding: Letter shift (+1=next letter), reverse, mirror, number substitution.
- * Blood Relations: Draw family tree. Father/mother/son/daughter. Maternal/paternal.
- * Direction sense: N-S-E-W. Right turn from North = East. Left from East = North.
- * Ranking/Order: From top: rank R. From bottom: N-R+1. Total = top_rank + bottom_rank - 1.
- * Calendar: Odd days concept. 1 ordinary year = 1 odd day. Leap = 2 odd days. 100 years = 5 odd days.
- * Clock: Angle = $|30H - 5.5M|$ degrees. Hands overlap 22 times in 24 hours (not 24).
- * Venn Diagrams: Intersection = common elements. Union = all elements. Complement = outside.
- * Syllogisms: All A are B + All B are C => All A are C. Some A are B: does NOT mean Some B are A (in some cases).
- * Seating arrangement: Linear or circular. Fix one person, arrange others relative.
- * Number series patterns: +n, xn, n^2 , n^2+1 , Fibonacci, Prime, alternating.
- * Mirror/Water image: Mirror(vertical) reverses L-R. Water(horizontal) reverses up-down.
- * Paper cutting/folding: Track folds systematically. Unfold in reverse order.

13. ENGLISH GRAMMAR - KEY RULES

- * Subject-Verb Agreement: Singular subject = singular verb. Each/Every/Neither = singular.
- * Tenses: Past (V2/had+V3), Present (V1/is+V-ing/has+V3), Future (will+V1/shall+V1).
- * Articles: a (before consonant sound), an (before vowel sound), the (specific/unique).
- * Active/Passive: Active: S+V+O. Passive: O+be+V3+by S. Tense of 'be' matches original tense.
- * Direct/Indirect speech: Remove quotes, add that, change pronouns and tenses back by one step.
- * Prepositions: at (time/point), on (surface/day), in (enclosed/month/year), by (deadline/agent).
- * Common errors: Between (2 things), Among (3+). Fewer (countable), Less (uncountable).
- * Idioms: Break the ice, Burn midnight oil, Beat around the bush, Blessing in disguise.
- * One-word substitution: Omnivore (eats all), Bibliophile (book lover), Ambidextrous (both hands).
- * Synonyms/Antonyms: Build vocabulary of 200 common words for competitive exams.
- * Comprehension: Read passage first. Then questions. Find answer IN the passage (not general knowledge).
- * Sentence correction: Check subject-verb, tense consistency, parallelism, modifier placement.
- * Fill in blanks: Context clues (but/although=contrast, and/moreover=addition, because/since=reason).
- * Para-jumbles: Find opening sentence (introduces topic), closing (concludes). Link pronouns to antecedents.

14. COMPUTER KNOWLEDGE - KEY FACTS

- * Hardware: CPU (ALU+CU), RAM (volatile), ROM (non-volatile), HDD/SSD (storage).
- * Memory hierarchy: Register > Cache > RAM > SSD > HDD (speed decreasing, size increasing).
- * RAM types: SRAM (cache, fast, expensive), DRAM (main memory, refresh needed).
- * ROM types: ROM, PROM, EPROM, EEPROM, Flash (increasing reprogrammability).
- * Input: Keyboard, Mouse, Scanner, Microphone, Webcam, Touchscreen, Joystick.
- * Output: Monitor, Printer, Speaker, Projector, Plotter.
- * Operating System: Windows, Linux, macOS. Functions: process mgmt, memory mgmt, file system, I/O.
- * MS Word: Ctrl+B (bold), Ctrl+I (italic), Ctrl+U (underline), Ctrl+S (save), Ctrl+Z (undo).
- * MS Excel: SUM, AVERAGE, COUNT, MAX, MIN, IF, VLOOKUP. Cell reference: A1 (relative), \$A\$1 (absolute).
- * MS PowerPoint: Slides, transitions, animations. Slide show: F5 (from beginning), Shift+F5 (current).
- * Internet: WWW, HTTP/HTTPS, URL, IP address, DNS, ISP, Bandwidth, Firewall.
- * Network: LAN (<1km), MAN (city), WAN (country/world). Topology: Star, Bus, Ring, Mesh.
- * Binary: 1 Byte = 8 bits. 1 KB = 1024 B. 1 MB = 1024 KB. 1 GB = 1024 MB. 1 TB = 1024 GB.
- * Programming: High-level (Python, Java, C++), Low-level (Assembly, Machine). Compiler vs Interpreter.
- * Database: DBMS, SQL (SELECT, INSERT, UPDATE, DELETE), Primary key, Foreign key.
- * Cyber security: Virus, Worm, Trojan, Phishing, Firewall, Encryption, VPN.
- * Cloud: IaaS, PaaS, SaaS. Examples: AWS (IaaS), Google App Engine (PaaS), Gmail (SaaS).
- * Full forms: CPU=Central Processing Unit, ALU=Arithmetic Logic Unit, RAM=Random Access Memory.
- * ASCII: A=65, a=97, 0=48. Unicode: supports international characters.
- * Generation of computers: 1st=Vacuum tubes, 2nd=Transistors, 3rd=ICs, 4th=VLSI, 5th=AI.

15. GENERAL AWARENESS - REVISION FRAMEWORK

- * INDIA: Capital=New Delhi, President, PM, CJI, CAG (check current holders on exam day).
- * AP State: Capital=Amaravati, CM, Governor, State bird=Rose-ringed Parakeet, Animal=Blackbuck.
- * APTRANSCO: Andhra Pradesh Transmission Corporation. HQ: Hyderabad. Under AP State Govt.
- * Constitution: Fundamental Rights (Art 12-35), DPSP (Art 36-51), Amendments (42nd, 44th, 73rd, 74th).
- * Economy: GDP, Fiscal deficit, Repo rate, Reverse repo (check latest RBI rates), CRR, SLR.
- * Awards: Nobel, Bharat Ratna, Padma awards (check latest recipients).
- * International: UN (HQ: NYC), WHO (Geneva), IMF/WB (Washington DC), UNESCO, UNICEF.
- * Sports: Cricket World Cup, Olympics, Asian Games (check recent winners).
- * Science: Recent ISRO missions, Nobel in Physics/Chemistry, Indian scientists.
- * Geography: Largest river, highest peak, important dams, national parks of AP/India.
- * History: Indian Independence 1947, Constitution adopted 1950, important leaders.
- * Current affairs: Focus on last 6 months. Government schemes, appointments, summits.
- * Telangana/AP specific: Recent state developments, power sector updates, new policies.
- * Power sector: National Grid, PGCIL, CEA, APGENCO, APSPDCL, APEPDCL.

KEY: Update GK on exam day morning: latest CM, PM, Governor, RBI Governor, important appointments.

16. 100 MOST COMMON FORMULA TRAPS

1. [CIRCUITS] RMS of sine = $0.707 \cdot V_m$, NOT $0.637 \cdot V_m$ (that is average). Form Factor = 1.11.
2. [CIRCUITS] $P = V \cos(\phi)$ uses RMS values, NOT peak. Using peak gives 2x the answer.
3. [CIRCUITS] Impedance $Z = \sqrt{R^2 + X^2}$, NOT $R + X$. Must square first.
4. [CIRCUITS] Conductance $G \neq 1/R$ when reactance present. $G = R/(R^2 + X^2)$.
5. [CIRCUITS] Series resonance: $Z=R$ (minimum), $I=\max$. Parallel: $Z=\max$, $I=\min$. Opposite!
6. [CIRCUITS] Q-factor series = $\omega L/R$. Q-factor parallel = $R/(\omega L)$. Inverse of each other.
7. [CIRCUITS] Voltage divider fails with load. Must account for parallel resistance of load.
8. [CIRCUITS] Current divider: I through $R_1 = I_{\text{total}} \cdot R_2/(R_1 + R_2)$. Uses OPPOSITE R in numerator.
9. [CIRCUITS] Time constant: RC circuit = RC . RL circuit = L/R . Not R/L .
10. [CIRCUITS] DC max power: $R_L = R_{Th}$. AC max power: $Z_L = Z_{Th}^*$ (conjugate). Different!
11. [CIRCUITS] Superposition: cannot superpose POWER. Must find V or I first, then P .
12. [CIRCUITS] Dependent sources are NEVER killed in Thevenin/Norton analysis.
13. [CIRCUITS] Star-Delta: $R_{\text{star}} = R_{\text{delta}}/3$ (balanced). Not $R_{\text{delta}} \cdot 3$.
14. [3-PHASE] $V_{\text{line}} = \sqrt{3} \cdot V_{\text{phase}}$ in STAR. $V_{\text{line}} = V_{\text{phase}}$ in DELTA.
15. [3-PHASE] 3-phase power = $\sqrt{3} \cdot V_L \cdot I_L \cdot \cos(\phi)$. Factor is $\sqrt{3}$, NOT 3.
16. [TRANSFORMER] EMF constant 4.44 is for SINE wave. For SQUARE wave: constant = 4.0.
17. [TRANSFORMER] VR sign: + for LAGGING, - for LEADING power factor.
18. [TRANSFORMER] Max efficiency when $Cu \text{ loss} = \text{Core loss}$. NOT at full load.
19. [TRANSFORMER] OC test = Core loss. SC test = $Cu \text{ loss}$. Never reversed.
20. [TRANSFORMER] Impedance referred: $Z_2 \text{ to primary} = Z_2/K^2$. Uses K SQUARED, not K .
21. [TRANSFORMER] All-day efficiency: Core loss for 24 hours, $Cu \text{ loss}$ only during loaded hours.
22. [TRANSFORMER] Transformer can step up VOLTAGE but not POWER. $V_A \text{ in} = V_A \text{ out}$ (ideal).
23. [DC MACHINE] Generator: $V = E - I_a R_a$ ($E > V$). Motor: $V = E_b + I_a R_a$ ($V > E_b$). Signs differ!
24. [DC MACHINE] Torque proportional to $\Phi \cdot I_a$, NOT speed. T and N are independent.
25. [DC MACHINE] Series motor: never run unloaded. Speed becomes dangerously high.
26. [DC MACHINE] Lap winding: $A=P$ (parallel paths=poles). Wave winding: $A=2$ always.
27. [DC MACHINE] Starting current: $I_{st} = V/R_a$ (very high). Starter limits this.
28. [INDUCTION MOTOR] $N_s = 120/f/P$. The constant is 120, not 60.
29. [INDUCTION MOTOR] Slip must be used as FRACTION (0.04) in formulas, not percentage (4%).
30. [INDUCTION MOTOR] Rotor $Cu \text{ loss} = s \cdot P_{ag}$. Not $s \cdot P_{\text{input}}$.
31. [INDUCTION MOTOR] T_{max} is INDEPENDENT of R_2 . Adding R_2 changes s_m but NOT T_{max} .
32. [INDUCTION MOTOR] Torque proportional to V^2 , not V . Half voltage = quarter torque.
33. [INDUCTION MOTOR] Star-delta starting: both current AND torque reduce to 1/3 of DOL.
34. [SYNC MACHINE] Over-excited sync motor = leading PF (like capacitor). Under-excited = lagging.
35. [SYNC MACHINE] Power angle $\delta > 90$ = unstable. Steady-state limit is $\delta = 90$.
36. [POWER SYS] Diversity Factor > 1 (always). All other load factors ≤ 1 .
37. [POWER SYS] Load Factor = Avg demand / Max demand, NOT Avg / Connected load.
38. [POWER SYS] Short line ABCD: $A=1$, $B=Z$, $C=0$, $D=1$. Shunt admittance is ZERO.
39. [POWER SYS] Ferranti effect: $V_{\text{receiving}} > V_{\text{sending}}$ at NO load. Due to line capacitance.
40. [POWER SYS] SIL = V^2/Z_c . At SIL: no reactive power, flat voltage profile.
41. [POWER SYS] Corona loss proportional to $(V - V_d)^2$. No corona below V_d .
42. [PER-UNIT] $Z_{\text{base}} = V_{\text{base}}^2/S_{\text{base}}$. Changes at each voltage level.
43. [PER-UNIT] Transformer impedance: SAME in p.u. on both sides. Key advantage.
44. [PER-UNIT] Base conversion: $Z_{pu_new} = Z_{pu_old} \cdot (S_{\text{new}}/S_{\text{old}}) \cdot (V_{\text{old}}/V_{\text{new}})^2$.
45. [FAULTS] 3-phase fault uses ONLY Z_1 . LG fault uses $Z_0 + Z_1 + Z_2$ in SERIES.
46. [FAULTS] LL fault: no Z_0 involved. Only Z_1 and Z_2 in series.
47. [FAULTS] LG fault is usually most severe for current. 3-phase for CB rating (MVA).
48. [FAULTS] $a = 1$ angle(120). $a^2 = 1$ angle(240). $a^3 = 1$. $1 + a + a^2 = 0$.
49. [PROTECTION] IDMT: higher PSM = LOWER operating time (faster for larger faults).
50. [PROTECTION] Differential relay: operates on $I_{\text{difference}}$, NOT I_{sum} .
51. [PROTECTION] CB making current = $2.55 \times I_{\text{rms}}$. Breaking current = I_{rms} of fault.
52. [PROTECTION] Mho relay: directional. Impedance relay: non-directional. Important difference.
53. [STABILITY] Equal area criterion: valid for single machine vs infinite bus ONLY.
54. [STABILITY] $P_{\text{max}} = V/E$. Increase E or decrease X for better stability.
55. [STABILITY] Higher inertia H = longer CCT = more stable. But slower response.
56. [CONTROL] System TYPE = # of integrators. System ORDER = highest power of s in char. eq. Different!

57. **[CONTROL]** Negative feedback: $TF = G/(1+GH)$. The + in denominator is for NEGATIVE feedback.
58. **[CONTROL]** Gain margin at PHASE crossover. Phase margin at GAIN crossover. Measured at different points!
59. **[CONTROL]** Both $GM > 0$ AND $PM > 0$ for stability. One alone is not sufficient.
60. **[CONTROL]** Root locus: # branches = # poles (n), NOT zeros.
61. **[CONTROL]** Asymptote angles = $(2k+1)*180/(n-m)$. Factor is (2k+1), not 2k.
62. **[CONTROL]** Type 0 system: finite SS error for step input = $1/(1+K_p)$. NOT zero.
63. **[CONTROL]** Lag compensator improves SS accuracy but REDUCES bandwidth.
64. **[CONTROL]** Lead compensator improves transient but INCREASES noise sensitivity.
65. **[CONTROL]** Routh criterion: zero/negative coefficient = UNSTABLE immediately.
66. **[CONTROL]** Breakaway point: occurs between two poles on real axis. Solve $dK/ds = 0$.
67. **[CONTROL]** Nyquist: # of encirclements of $-1+j0$ determines stability.
68. **[CONTROL]** Phase margin is measured from -180 line, NOT from 0.
69. **[CONTROL]** Overshoot depends on damping ratio only: $OS\% = e^{-\pi \zeta / \sqrt{1-\zeta^2}} * 100$.
70. **[CONTROL]** Settling time (2%): $t_s = 4/(\zeta \omega_n)$. Rise time = $(\pi - \phi)/\omega_d$.
71. **[ELECTRONICS]** $\alpha = I_{C/I_E} \approx 0.98$. $\beta = I_{C/I_B} \approx 100$. $\alpha \ll \beta$.
72. **[ELECTRONICS]** $\beta = \alpha/(1-\alpha)$. Small change in α causes LARGE change in β .
73. **[ELECTRONICS]** CE amplifier: 180 degree phase shift. CB and CC: NO phase shift.
74. **[ELECTRONICS]** PMMC reads average (zero for AC). Moving Iron reads TRUE RMS.
75. **[ELECTRONICS]** Rectifier instrument reads average but CALIBRATED for sine RMS (multiply by 1.11).
76. **[ELECTRONICS]** PIV of bridge rectifier = V_m . PIV of center-tap = $2V_m$. Different!
77. **[ELECTRONICS]** Half-wave ripple factor = 1.21 (more AC than DC). Full-wave = 0.482.
78. **[ELECTRONICS]** FET: $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$. Square law device.
79. **[ELECTRONICS]** MOSFET: gate current = 0 (extremely high input impedance). Unlike BJT.
80. **[POWER ELEC]** SCR: $I_{latching} > I_{holding}$. Latching > Holding current always.
81. **[POWER ELEC]** Full-bridge rectifier $V_{dc} = 2V_m \cos(\alpha)/\pi$ for RL load (continuous conduction).
82. **[POWER ELEC]** V_{dc} decreases as firing angle α increases. At $\alpha=90$: $V_{dc}=0$.
83. **[POWER ELEC]** Buck: $V_{out} = D*V_{in}$ (step-down). Boost: $V_{out} = V_{in}/(1-D)$ (step-up).
84. **[POWER ELEC]** Square wave inverter harmonics: 3rd, 5th, 7th... (only ODD harmonics).
85. **[POWER ELEC]** dB voltage gain = $20 \log(V_2/V_1)$. dB power gain = $10 \log(P_2/P_1)$. Factor 20 vs 10!
86. **[MEASUREMENT]** Maxwell bridge: for LOW Q coils ($Q=1-10$). Hay bridge: for HIGH Q coils ($Q>10$).
87. **[MEASUREMENT]** Schering bridge: for HIGH VOLTAGE capacitance/insulation testing.
88. **[MEASUREMENT]** Wien bridge: frequency measurement. $f = 1/(2\pi RC)$ at balance.
89. **[MEASUREMENT]** Instrument accuracy is % of FSD, not of reading. Worst at low readings.
90. **[MEASUREMENT]** CRO Lissajous: f_y/f_x = tangencies on horizontal / tangencies on vertical.
91. **[APTITUDE]** Percentage increase then same decrease: NET LOSS. 20% up then 20% down = 4% loss.
92. **[APTITUDE]** Average speed for equal distances at S_1 and S_2 : $V_{avg} = 2*S_1*S_2/(S_1+S_2)$, NOT $(S_1+S_2)/2$.
93. **[APTITUDE]** Time and work: RATES add, not TIMES. If A=10 days, B=15 days: together = 6 days.
94. **[APTITUDE]** Probability: $P(A \text{ or } B) = P(A)+P(B)-P(A \text{ and } B)$. Don't forget to subtract intersection.
95. **[APTITUDE]** CI: Amount = $P*(1+R/100)^n$. CI = Amount - P. NOT $P*R*n/100$ (that is SI).
96. **[UNITS]** 1 HP = 746 W. 1 kWh = 3.6 MJ = 3600 kJ. 1 cal = 4.186 J.
97. **[UNITS]** 1 Wb = 1 V-s. 1 H = 1 Wb/A. 1 F = 1 C/V. Check dimensional consistency.
98. **[UNITS]** Angular frequency ω (rad/s) != frequency f (Hz). $\omega = 2\pi f$.
99. **[UNITS]** RPM to rad/s: multiply by $2\pi/60$. rad/s to RPM: multiply by $60/(2\pi)$.
100. **[GENERAL]** No negative marking = ATTEMPT ALL. Even random guess has 25% chance.

17. MASTER FORMULA TABLES (QUICK-REFERENCE)

MACHINES MASTER TABLE

MACHINE	KEY EQUATION	EFFICIENCY CONDITION	KEY CHARACTERISTIC
Transformer	$E = 4.44fN\Phi$	Cu loss = Core loss	VR: +lag, -lead
DC Generator	$E = P\Phi ZN/(60A)$	Variable = Constant loss	$V = E - IaRa$
DC Motor	$E_b = V - IaRa$	Variable = Constant loss	$T = Kt\Phi Ia$
Induction Motor	$N_s = 120f/P$	Min losses at opt slip	Pag:Pcu:Pm = 1:s:1-s
Sync Generator	$E = 4.44Kw\Phi T$	VR depends on PF	$P = VE\sin(d)/X_s$
Sync Motor	Same as generator	V-curves / Inv-V	Over-excited=leading

POWER SYSTEM FAULT TABLE

FAULT	SEQUENCE CONNECTION	I_fault	SEVERITY
3-phase (LLL)	Z1 only	$V_f/Z1$	Reference
SLG (LG)	Z0+Z1+Z2 series	$3V_f/(Z0+Z1+Z2)$	Usually highest I
LL	Z1+Z2 series	$\sqrt{3}V_f/(Z1+Z2)$	Lowest I
LLG	Z1 + Z0//Z2	$3V_f/(Z1+Z0//Z2)$	2nd highest

RECTIFIER COMPARISON TABLE

PARAM	HALF-WAVE	FW CENTER-TAP	FW BRIDGE	3-PH BRIDGE
Vdc	0.318Vm	0.636Vm	0.636Vm	1.654Vm
Ripple	1.21	0.482	0.482	0.04
PIV	Vm	2Vm	Vm	Vm
Efficiency	40.6%	81.2%	81.2%	99.8%
Diodes	1	2	4	6
Ripple freq	f	2f	2f	6f

CONTROL SYSTEM SUMMARY

CONCEPT	FORMULA/RULE	QUICK CHECK
Steady-state error	$ess = 1/(1+Kp)$ [step, Type 0]	Type >= input type => ess=0
Routh stability	All 1st col positive	Missing coeff => unstable
Gain Margin	-20log G at phase=-180	GM>0 for stable
Phase Margin	180+angle(G) at G =0dB	PM>0 for stable
Root Locus asymp.	$(2k+1)*180/(n-m)$	Centroid=(sum_p - sum_z)/(n-m)
2nd order	$\omega_n, \zeta, \omega_d = \omega_n \sqrt{1-\zeta^2}$	$OS\% = \exp(-\pi\zeta/\sqrt{1-\zeta^2})*100$

18. HIGH-PRIORITY FORMULA LIST (Top 80 - Revise Daily)

1. $V=IR$ | $P=VI=I^2R=V^2/R$ | $E=Pt$
2. $R_{series}=R1+R2$ | $R_{parallel}=R1*R2/(R1+R2)$ | VDR: $V_k=V*R_k/R_{total}$
3. Thevenin: V_{Th} , R_{Th} , $I_L=V_{Th}/(R_{Th}+R_L)$ | Norton: $I_N=V_{Th}/R_{Th}$
4. Max power (DC): $R_L=R_{Th}$, $P_{max}=V_{Th}^2/(4R_{Th})$ | (AC): $Z_L=Z_{Th}^*$
5. $V_{rms}=0.707V_m$ | $V_{avg}=0.637V_m$ | $FF=1.11$ | $CF=1.414$
6. $Z=R+jX$ | $|Z|=\sqrt{R^2+X^2}$ | $\phi=\arctan(X/R)$
7. $X_L=2\pi fL$ | $X_C=1/(2\pi fC)$ | $f_r=1/(2\pi\sqrt{LC})$
8. $Q_{series}=wL/R=1/(wCR)$ | $BW=f_r/Q=R/(2\pi L)$ | $Q_{parallel}=R/(wL)$
9. $P=VI\cos(\phi)$ | $Q=VI\sin(\phi)$ | $S=VI$ | $PF=P/S=\cos(\phi)$
10. 3-ph: $P=\sqrt{3}*V_L*I_L*\cos(\phi)$ | Star: $V_L=\sqrt{3}*V_{ph}$ | Delta: $I_L=\sqrt{3}*I_{ph}$
11. 2-Wattmeter: $P=W1+W2$ | $\tan(\phi)=\sqrt{3}*(W1-W2)/(W1+W2)$
12. $\tau_{RL}=L/R$ | $\tau_{RC}=RC$ | $v(t)=V_f+(V_i-V_f)*e^{-t/\tau}$
13. $M=k*\sqrt{L1*L2}$ | Aiding: $L_{eq}=L1+L2+2M$ | Opposing: $L1+L2-2M$
14. $E_{transformer}=4.44*f*N*\Phi$ | $K=N2/N1=V2/V1=I1/I2$
15. $VR\%=(I*Req*\cos(\phi) \pm I*Xeq*\sin(\phi))/V \times 100$ [+lag, -lead]
16. $\eta_{transformer}=xScos(\phi)/[xScos(\phi)+Pi+x^2*Pcu]$ | Max: $x=\sqrt{Pi/Pcu}$
17. $E_{dc}=P*\Phi*N/(60A)$ | $T=K*\Phi*I_a$ | $E_b=V-I_aR_a$ [motor]
18. $N_s=120f/P$ | $s=(N_s-N_r)/N_r$ | $f_r=s*f$ | $N_r=N_s(1-s)$
19. $P_{ag}=P_{rcu}$: $P_{mech} = 1:s:(1-s)$ | $P_{rcu}=s*P_{ag}$ | $P_{mech}=(1-s)*P_{ag}$
20. T_{max} at $s=R2/X2$ | T_{max} independent of $R2$ | T proportional to V^2
21. Sync: $E=4.44*K_w*f*\Phi*T$ | $K_w=K_p*K_d$ | $P=VE*\sin(\delta)/X_s$
22. $LF=Avg/Max$ | $DF=MaxD/ConnLoad$ | $DivF=Sum_indiv/System_max (>1)$
23. Short line: $V_s=V_r+I_rZ$ | $VR\%=I_r(R\cos+X\sin)/V_r$
24. $Z_c=\sqrt{L/C}$ | $SIL=V_L^2/Z_c$
25. $Z_{pu}=Z_{actual}/Z_{base}$ | $Z_{base}=V_{base}^2/S_{base}$ | $I_{base}=S_{base}/(\sqrt{3}*V_{base})$
26. LG: $I_f=3V_f/(Z0+Z1+Z2)$ | 3-ph: $I_f=V_f/Z1$ | LL: $I_f=\sqrt{3}*V_f/(Z1+Z2)$
27. IDMT: $t=k*TMS/(PSM^n-1)$ | $PSM=I_{fault}/I_{setting}$
28. Swing: $M*d^2\delta/dt^2=P_m-P_e$ | EAC: $A1 \leq A2$ for stability
29. CLTF= $G/(1+GH)$ | $ess=1/(1+K_p)$ [step] | $ess=1/K_v$ [ramp]
30. Routh: all 1st col positive => stable | #sign changes = #RHP roots
31. $GM=-20\log|G(jwpc)|$ | $PM=180+angle(G(jwgc))$
32. RL asymptotes: $(2k+1)*180/(n-m)$ | Centroid= $(\Sigma p-\Sigma z)/(n-m)$
33. $F_t=Ma+Mgsin(\theta)+r$ | $E_{sp}=E/(M*D)$ Wh/tonne-km | $V_s=D/(Trun+Tstop)$
34. $H=I^2Rt$ | Dielectric: P proportional to $f*V^2*\epsilon*\tan(\delta)$
35. Bridge: Wheatstone $R1R3=R2R_x$ | Schering: $C_x=C_s*R2/R1$ | Wien: $f=1/(2\pi RC)$
36. $\alpha=\beta/(1+\beta)$ | $\beta=\alpha/(1-\alpha)$ | $I_E=I_B+I_C$ | $g_m=I_C/V_T$
37. $ID=IDSS*(1-V_{GS}/V_P)^2$ | $g_m=-2IDSS*(1-V_{GS}/V_P)/V_P$
38. HW: $V_{dc}=V_m/\pi$, $\gamma=1.21$ | FW: $V_{dc}=2V_m/\pi$, $\gamma=0.482$
39. SCR: $I_L > I_H$ | Controlled rect: $V_{dc}=2V_m*\cos(\alpha)/\pi$ [1-ph bridge]
40. Buck: $V_o=DV_{in}$ | Boost: $V_o=V_{in}/(1-D)$ | $D=T_{on}/T$

19. FORMULA-TO-QUESTION-TYPE MAPPING

FORMULA/TOPIC	USUALLY ASKED AS	DIFFICULTY	TIME (sec)
Ohm law, KVL, KCL	Numerical (find $V/I/R$)	Easy	30-45
Thevenin/Norton	Numerical (find V_{Th} , R_{Th})	Medium	60-90
Max Power Transfer	Numerical (find P_L max)	Easy-Medium	45-60
RMS/Average values	Conceptual + Numerical	Easy	20-30
Series/Parallel resonance	Numerical (fr, Q, BW)	Medium	45-60
3-Phase power	Numerical	Easy-Medium	30-60
2-Wattmeter method	Numerical (find PF)	Medium	60
Transients (RC/RL)	Numerical (find $v(t)$, $i(t)$)	Medium	60-90
Transformer EMF	Numerical	Easy	30
Transformer VR	Numerical	Medium	45-60
Transformer efficiency	Numerical	Medium	60-90
DC Motor speed/torque	Numerical	Medium	60
IM Slip/Speed/Frequency	Numerical	Easy	30
IM Power flow (1:s:1-s)	Numerical	Medium	45-60
IM Max torque condition	Conceptual + Numerical	Medium	45
Sync machine power-angle	Numerical	Medium-Hard	60-90
Load factors	Numerical	Easy	30
Transmission line VR	Numerical	Medium	60
Per-unit calculation	Numerical	Medium	60-90
Fault current (LG/3-ph)	Numerical	Medium-Hard	90
IDMT relay time	Numerical	Medium	60
SS error (Type/Kp/Kv)	Numerical + Conceptual	Medium	45
Routh array	Conceptual (stability)	Medium	60-90
Bode GM/PM	Conceptual + Numerical	Medium-Hard	60-90
Root locus rules	Conceptual	Medium	45
Rectifier Vdc/ripple	Numerical + Conceptual	Easy	30
BJT alpha/beta	Numerical	Easy	20-30
SCR characteristics	Conceptual	Easy	20
Chopper duty cycle	Numerical	Easy	30
Bridge balance	Numerical	Medium	45-60
Instrument type/reading	Conceptual	Easy	20
Aptitude (% , SI/CI)	Numerical	Easy-Medium	60-90
Reasoning (series/analogy)	Pattern recognition	Easy-Medium	30-60

20. YOUR 6-DAY FINAL REVISION PLAN

21 August (Thu) to 26 August (Tue) 2026

DAY 1 - Thursday 21 August: ELECTRIC CIRCUITS + CONTROL SYSTEMS

TIME	TOPIC	WHAT TO DO	TARGET
6:00-8:00 AM	DC Circuits	Ohm, KVL, KCL, Series/Parallel, VDR, CDR, Star-Delta	All basic formulas revised
8:30-10:30	Network Theorems	Thevenin, Norton, Max Power, Superposition	10 numericals solved
11:00-1:00 PM	AC Fundamentals + RLC	Impedance, Phasor, Resonance, Q-factor, BW	All AC formulas + 10 numericals
2:00-4:00	3-Phase + Transients	3-phase power, 2-wattmeter, RC/RL transients	Star-Delta table memorized
4:30-6:30	Control Systems	TF, Mason, SS error, Routh, Bode, Root Locus	Type-error table memorized
7:00-8:30	Practice MCQs	25 MCQs from Circuits + 15 from Control	80% accuracy target
9:00-10:00	Formula Review	Re-read all formulas covered today. Mark weak areas.	Identify gaps

DAY 2 - Friday 22 August: ELECTRICAL MACHINES

TIME	TOPIC	WHAT TO DO	TARGET
6:00-8:30 AM	Transformers	EMF, VR, Efficiency, Max eta, OC/SC, Autotransformer	All transformer formulas
9:00-11:00	DC Machines	EMF, Torque, Speed, Motor/Gen equations, Speed control	Shunt vs Series clear
11:30-2:00 PM	Induction Motor	Ns, slip, fr, power flow, torque, Tmax, starting	1:s:(1-s) ratio mastered
2:30-4:30	Synchronous Machines	EMF, Kp, Kd, VR, Power-angle, V-curves	Over/under excitation clear
5:00-6:30	Single-phase Motors	Double revolving field, types, applications	All types memorized
7:00-9:00	Practice MCQs	30 MCQs from all machines topics	80% accuracy target
9:30-10:30	Formula + Theory review	Re-read machines formulas. Key theory points.	All characteristics clear

DAY 3 - Saturday 23 August: POWER SYSTEMS

TIME	TOPIC	WHAT TO DO	TARGET
6:00-8:00 AM	Generation + Economics	Load factor, Demand factor, Diversity, Economic dispatch	All factors memorized
8:30-10:30	Transmission Lines	Short/Medium/Long, VR, ABCD, Corona, SIL	ABCD table memorized
11:00-1:00 PM	PU System + Faults	Base conversion, LG/LL/LLG/3-phase fault currents	Fault table memorized
2:00-4:00	Protection	IDMT, Differential, Distance relays, CB ratings	Relay types clear
4:30-6:00	Stability + Cables/Insulators	Swing eq, EAC, String efficiency	EAC concept clear
6:30-8:30	Practice MCQs	30 MCQs from all Power Systems topics	75% accuracy target
9:00-10:00	Formula Review	Re-read all power system formulas	Identify weak areas

DAY 4 - Sunday 24 August: MEASUREMENTS + ELECTRONICS + POWER ELECTRONICS

TIME	TOPIC	WHAT TO DO	TARGET
6:00-8:00 AM	Measurement Bridges	All 7+ bridges: balance conditions, what they measure	Bridge table memorized
8:30-10:00	Instruments + CRO	PMMC, MI, Dynamo, CRO measurements, Q-meter	Instrument characteristics clear
10:30-12:30	Analog Electronics	Diodes, Rectifiers, BJT, FET, Op-Amp	Rectifier table memorized
1:00-2:30 PM	Digital Electronics	Logic gates, Boolean, Flip-flops, ADC/DAC, Number systems	Gate table + De Morgan clear
3:00-5:00	Power Electronics	SCR, Rectifiers (controlled), Choppers, Inverters	Chopper formulas memorized
5:30-7:30	Practice MCQs	30 MCQs covering all 3 subjects	75% accuracy target
8:00-9:30	Review weak areas	Revisit any formulas you got wrong in MCQs	All gaps filled

DAY 5 - Monday 25 August: COMMON SECTION (30 marks)

TIME	TOPIC	WHAT TO DO	TARGET
6:00-8:00 AM	Quant Aptitude	%, SI/CI, Speed-Distance, Ratio, Probability, Mensuration	All shortcut formulas
8:30-10:00	Reasoning	Analogies, Series, Classification, Coding, Blood relations	Pattern recognition speed
10:30-12:00	English	Grammar rules, Vocabulary, Comprehension practice	Common error patterns
12:30-1:30 PM	Computer Knowledge	Hardware, Software, MS Office, Internet, Networks	Key facts memorized
2:00-3:30	General Awareness	Current affairs, Polity, Economy, Geography, AP specific	Recent appointments/events
4:00-6:00	FULL MOCK TEST	Attempt 100 questions in 120 minutes. All subjects.	Score 70+ target
6:30-8:30	Mock Analysis	Review wrong answers. Identify patterns. Note weak formulae	Know exact weaknesses
9:00-10:00	Final formula read	Read through High-Priority Formula list (Section 18)	Confidence building

DAY 6 - Tuesday 26 August: EXAM DAY

TIME	ACTIVITY	DETAILS
5:00 AM	Wake up	Light exercise, shower, good breakfast (carbs + protein)
6:00-7:00	Ultra-Revision Sheet ONLY	Read ONE-PAGE sheet (Section 22). Nothing new.
7:00-7:30	Top 20 Traps	Read traps #1-20 from Section 16. Most critical ones.
7:30-8:00	Logistics check	Admit card, ID proof, water bottle, watch. Pack bag.
8:00-8:30	Travel to center	Arrive 30 min before gate opens. Stay calm.
8:30-9:00	At center	Deep breathing. No new study. Trust your preparation.
EXAM TIME	2 hours	Execute strategy from Section 21. Attempt ALL 100 questions.

GOLDEN RULES FOR DAY 6:

- * NO new topics. Only revision of already-studied material.
- * NO heavy meals. Light breakfast. Stay hydrated.
- * NO discussion with friends about preparation (increases anxiety).
- * Do NOT study until the last minute. Stop 30 minutes before exam.
- * Positive self-talk: 'I have prepared well. I will execute my strategy.'

21. FINAL 2-HOUR EXAM STRATEGY

TIME ALLOCATION (120 minutes, 100 questions)

PHASE	TIME	QUESTIONS	WHAT TO DO
Quick scan	0-5 min	All 100	Read all questions. Mark easy/hard mentally.
Easy pass	5-40 min	~40 easy Qs	Attempt all easy questions FIRST. Build confidence.
Medium pass	40-85 min	~35 medium Qs	Solve moderate questions. Use formulas carefully.
Hard pass	85-110 min	~15 hard Qs	Attempt harder ones. Skip if >3 min per Q.
Review + Guess	110-120 min	Remaining	Guess ALL unanswered. Review flagged answers.

SECTION-WISE STRATEGY

SECTION	MARKS	TIME (min)	ATTEMPT ORDER	STRATEGY
Aptitude + Reasoning	13	15	1st (warm-up)	Quick wins. Build confidence.
English + GK + Comp	17	12	2nd	Read carefully. Eliminate 2 options.
Electric Circuits	10	15	3rd	Formula-based. Quick numericals.
Electrical Machines	15	20	4th	Highest marks. Transformer+IM focus.
Power Systems	18	25	5th	Most formulas. PU+Faults important.
Control Systems	12	15	6th	SS error, Routh, Bode.
Measurements	5-8	8	7th	Bridge formulas. Quick.
Electronics + PE	10-12	10	8th	Rectifiers, BJT, Chopper formulas.

CRITICAL EXAM TECHNIQUES

- * **Exploit No-Negative-Marking:** Attempt ALL 100 questions. Even random guessing gives 25 marks on average. An educated guess after eliminating 2 wrong options gives 50%. NEVER leave any question blank.
- * **Elimination Method:** For conceptual MCQs, eliminate obviously wrong options first. Even eliminating 1 option improves your odds from 25% to 33%. Eliminating 2 gives 50%.
- * **Dimensional Analysis:** Check if your answer has correct units. If question asks for power (W) and your answer has Ohm-Amperes, something is wrong. Quick sanity check.
- * **Estimation/Approximation:** For complex calculations, estimate the answer range. If options are 10, 20, 30, 40 and your quick estimate gives ~18, choose 20. Saves time vs exact calculation.
- * **Back-Substitution:** For some problems, plug each option into the equation and check which satisfies. Faster than solving forward, especially for complex equations.
- * **Sign Conventions:** Write down sign conventions BEFORE starting calculation. Lagging=+, Leading=-. Motor: $V=E_b+I_aR_a$. Generator: $V=E-I_aR_a$.
- * **Unit Conversions:** Convert ALL quantities to SI units FIRST. RPM to rad/s: multiply by $2\pi/60$. kV to V: multiply by 1000. MW to W: multiply by 10^6 .
- * **Avoid Silly Mistakes:** Read question twice. Check: is it asking for LINE or PHASE? RMS or PEAK? Efficiency or regulation? Motor or generator? The difference between right and wrong is often ONE word.
- * **When to Skip:** If a numerical requires >3 minutes and you are not confident of the approach, SKIP IT. Come back later. Mark it clearly. Better to solve 3 easy questions in that time.
- * **Final 10 Minutes:** STOP solving new problems. Review your answers. Check if any question is unanswered. Make educated guesses for all blanks. Submit confidently.

22. ONE-PAGE ULTRA-REVISION SHEET

Print this page. Keep it with you. Read 1 hour before exam.

CORE FORMULAS (Read in 15 minutes)

$V=IR$ | $P=VI\cos(\phi)$ | $Q=VI\sin(\phi)$ | $S=VI$ | $PF=\cos(\phi)=P/S$
3-ph: $P=\sqrt{3}*VL*IL*\cos(\phi)$ | Star: $VL=\sqrt{3}*V_{ph}$ | Delta: $IL=\sqrt{3}*I_{ph}$
2WM: $P=W1+W2$ | $\tan(\phi)=\sqrt{3}*(W1-W2)/(W1+W2)$
 $f_r=1/(2\pi*\sqrt{LC})$ | $Q_{ser}=wL/R$ | $Q_{par}=R/(wL)$ | $BW=f_r/Q$
 $\tau_{RL}=L/R$ | $\tau_{RC}=RC$ | 63.2% at 1τ | 99.3% at 5τ
 $E_{xfmr}=4.44fN\Phi$ | $K=N2/N1=V2/V1=I1/I2$
 $VR\%=(IR\cos\phi - IX\sin\phi)/V \times 100$ | +lag -lead | Max η : $Cu=Core\ loss$
 $E_{dc}=P\Phi ZN/(60A)$ | $T=K\Phi I_a$ | Motor: $V=E_b+I_a R_a$ | Gen: $V=E-I_a R_a$
 $N_s=120f/P$ | $s=(N_s-N_r)/N_s$ | $f_r=sf$ | $N_r=N_s(1-s)$
Pag:Prcu:Pm = 1:s:(1-s) | $s_m=R2/X2$ | Tmax indep. of R2 | T prop V^2
Sync: $P=VE*\sin(d)/X_s$ | $P_{max}=VE/X_s$ at $d=90$ | Overexcited=leading PF
PU: $Z_{base}=V_{base}^2/S_{base}$ | $I_{base}=S_{base}/(\sqrt{3}*V_{base})$
3-ph fault: $I_f=V_f/Z1$ | LG: $I_f=3V_f/(Z0+Z1+Z2)$ | LL: $I_f=\sqrt{3}*V_f/(Z1+Z2)$
IDMT: $t=k*TMS/(PSM^n-1)$ | $PSM=I_{fault}/I_{setting}$
CLTF= $G/(1+GH)$ | $ess_step=1/(1+K_p)$ | $ess_ramp=1/K_v$
GM at phase crossover | PM at gain crossover | Both > 0 = stable
Routh: all 1st col positive = stable | missing coeff = unstable
HW: $V_{dc}=V_m/\pi$, $\gamma=1.21$ | FW: $V_{dc}=2V_m/\pi$, $\gamma=0.482$
 $\alpha=\beta/(1+\beta)$ | $\beta=\alpha/(1-\alpha)$ | FET: $ID=IDSS*(1-V_{GS}/V_P)^2$
SCR: $IL>IH$ | Buck: $V_o=DV_{in}$ | Boost: $V_o=V_{in}/(1-D)$ | Rect: $V_{dc}=2V_m*\cos(a)/\pi$

NUMERICAL VALUES TO MEMORIZE

$\sqrt{2}=1.414$ | $\sqrt{3}=1.732$ | $1/\sqrt{3}=0.577$ | $\pi=3.14159$
 $\sin 30=0.5$, $\cos 30=0.866$, $\tan 30=0.577$ | $\sin 45=\cos 45=0.707$ | $\sin 60=0.866$, $\cos 60=0.5$, $\tan 60=1.732$
50Hz speeds: 2P=3000, 4P=1500, 6P=1000, 8P=750, 10P=600, 12P=500 rpm
 $RMS=0.707*Peak$ | $Avg=0.637*Peak$ | $FF=1.11$ | $CF=1.414$ | 1HP=746W | 1kWh=3.6MJ

TOP 10 TRAPS TO AVOID (Last-minute reminders)

1. Use SLIP as fraction (0.04), not percentage (4%)
2. VR sign: + for LAGGING, - for LEADING
3. Max efficiency: $Cu\ loss = Core\ loss$ (not at full load)
4. 3-phase power always has $\sqrt{3}$ factor, not 3
5. Torque proportional to $\Phi*I_a$, NOT speed
6. Series resonance $Z=\min$, Parallel $Z=\max$ (OPPOSITE)
7. GM at PHASE crossover, PM at GAIN crossover
8. System TYPE != System ORDER (integrators vs s-power)
9. LG fault: $Z0+Z1+Z2$ SERIES. LL fault: $Z1+Z2$ only (no $Z0$)
10. NO NEGATIVE MARKING = ATTEMPT ALL 100 QUESTIONS!

YOUR TARGET: 65+ Electrical + 25+ Common = 90+ Total

You have prepared thoroughly. Trust your preparation. Execute the strategy. Stay calm. You've got this!

23. PREVIOUS-EXAM REPEATED THEORY KEY POINTS

These topics have appeared as conceptual/theory MCQs in previous APTRANSCO/APGENCO/TSTRANSCO AEE exams and similar state-level electrical engineering competitive exams. Memorize these facts.

TRANSFORMER THEORY

- * Transformer works on mutual induction principle (NOT self-induction).
- * Ideal transformer: no losses, no leakage flux, no resistance, infinite permeability core.
- * Core loss has two components: Hysteresis loss (proportional to $f \cdot B_{\max}^{1.6}$) and Eddy current loss (proportional to $f^2 \cdot B_{\max}^2$).
- * To reduce eddy current: use LAMINATED core (thin silicon steel sheets, 0.35mm).
- * Transformer oil: provides insulation AND cooling. Mineral oil with BDV > 30kV.
- * Buchholz relay: ONLY for oil-immersed transformers. Gas-actuated. Float (minor fault alarm) + Baffle (major fault trip).
- * Parallel operation conditions: same voltage ratio, same polarity, same phase sequence, same percentage impedance.
- * Tap changing: on-load (OLTC) for continuous voltage control. Off-load for seasonal adjustment.
- * Scott connection: converts 3-phase to 2-phase using two transformers (teaser + main).
- * Cooling methods: ONAN (natural), ONAF (forced air), OFAF (forced oil+air), OFWF (forced oil+water).
- * Vector groups: Yd1, Yd11, Yy0, Dd0, etc. Number indicates phase shift in units of 30 degrees.
- * Third harmonic in transformer: circulates in Delta winding, absent from line currents.

DC MACHINE THEORY

- * DC machine converts mechanical energy to electrical (generator) or electrical to mechanical (motor).
- * Commutator: mechanical rectifier in generator, mechanical inverter in motor. Converts AC in armature to DC at terminals.
- * Armature reaction: cross-magnetizing component shifts MNA by angle theta. Demagnetizing at large angles.
- * Compensating winding: in pole face, carries armature current in OPPOSITE direction. Neutralizes armature reaction.
- * Interpoles (commutating poles): small poles between main poles. Carry armature current. Improve commutation.
- * Swinburne test: NO-LOAD test. Gives constant losses. Cannot test commutation or temperature rise.
- * Hopkinson (back-to-back) test: two IDENTICAL machines coupled. One motor, one generator. Requires only loss power from supply.
- * Speed control: Shunt motor - armature resistance (below base), field weakening (above base), Ward-Leonard (full range).
- * Series motor applications: traction, cranes, hoists (high starting torque needed).
- * Compound motor: cumulative (series flux aids shunt flux) or differential (opposes). Cumulative is more common.

INDUCTION MOTOR THEORY

- * Works on principle of rotating magnetic field (Ferraris principle).
- * Rotor MUST run slower than synchronous speed to produce torque (needs relative motion = slip).
- * At synchronous speed: no relative motion, no induced EMF, no current, no torque.
- * Squirrel cage: simple, rugged, low maintenance, low starting torque. Most widely used industrial motor.
- * Slip ring (wound rotor): external resistance can be added. Higher starting torque. Speed control possible. More expensive.
- * Starting methods: DOL (small motors), Star-Delta ($I_{st}=1/3$), Autotransformer ($I_{st}=x^2$), Soft starter, VFD.
- * Crawling: motor runs at 1/7th of synchronous speed due to 7th harmonic torque component.
- * Cogging: motor refuses to start if stator slots = integer multiple of rotor slots (magnetic locking).
- * Double cage rotor: outer cage (high R, low X) for starting, inner cage (low R, high X) for running.
- * Deep bar rotor: similar to double cage effect. Skin effect at starting increases effective resistance.
- * V/f control: maintains constant flux ratio. Most popular speed control for squirrel cage motors.
- * Regenerative braking: motor speed > synchronous speed, acts as generator, returns energy to supply.
- * Plugging: reversing phase sequence. Very high braking torque but wastes energy.

SYNCHRONOUS MACHINE THEORY

- * Synchronous machine runs EXACTLY at synchronous speed ($N_s = 120f/P$). No slip.
- * Not self-starting as a motor. Needs damper winding or external starting method.
- * Damper winding: short-circuited copper bars in pole face. Provides starting torque AND damps hunting oscillations.
- * Over-excited sync motor: acts as CAPACITOR (leading PF, generates reactive power). Used as synchronous condenser.
- * Under-excited sync motor: acts as INDUCTOR (lagging PF, absorbs reactive power).
- * V-curves: I_{armature} vs I_{field} at constant load. U-shaped. Minimum at unity PF.
- * Inverted V-curves: PF vs I_{field} . Peak (unity PF) in middle.
- * Dark lamp test and synchroscope: used for synchronization of alternator to grid.
- * Hunting: oscillation of rotor about mean position. Caused by sudden load changes. Damper winding reduces it.
- * Synchronous impedance method (EMF method): gives PESSIMISTIC (higher) regulation due to saturation ignored.

POWER SYSTEM THEORY

- * Transmission voltage levels: 11kV, 33kV, 66kV, 110kV, 132kV, 220kV, 400kV, 765kV (India).
- * Higher transmission voltage = lower current = lower I^2R losses = more efficient.
- * Bundle conductors: 2/3/4 conductors per phase. Reduces corona, reduces reactance, increases SIL.
- * ACSR conductor: Aluminum Conductor Steel Reinforced. Steel core for strength, Al for conductivity.
- * Sag: increases with temperature, conductor weight, span length. Decreases with tension.
- * Earthing: Solid, Resistance, Reactance, Peterson coil (resonant grounding). Solid = highest fault current.
- * Peterson coil: tunes out capacitive ground fault current. $I_L = I_C$ at resonance. Zero fault current ideally.
- * Auto-reclosing: 80-90% of faults are temporary (lightning). CB opens and recloses automatically.
- * Under-frequency relay: trips load or generator to prevent system collapse during frequency drop.
- * HVDC advantages: no charging current, no stability limit, asynchronous interconnection, less conductor material.
- * FACTS devices: SVC, STATCOM, TCSC, UPFC. Improve stability, control voltage, increase power transfer.
- * Load frequency control (LFC): maintains frequency at 50 Hz by adjusting generator output.

PROTECTION THEORY

- * Primary protection: first line of defense. Backup protection: operates if primary fails.
- * Protection zones: overlapping to ensure no unprotected area (blind spot).
- * CT (Current Transformer): steps DOWN current. Connected in SERIES. Secondary never open-circuited.
- * PT (Potential Transformer): steps DOWN voltage. Connected in PARALLEL. Secondary can be open-circuited.
- * Overcurrent relay: most basic. IDMT characteristic: faster for larger faults.
- * Directional relay: can distinguish between fault direction. Used in ring/parallel systems.
- * Distance relay zones: Zone 1 (80% line, instantaneous), Zone 2 (120%, 0.3s delay), Zone 3 (backup, 1s).
- * Differential protection: compares entering and leaving currents. For transformers, generators, busbars.
- * Restricted earth fault: sensitive ground fault protection. Detects faults that differential might miss.
- * Lightning arrester/surge arrester: protects equipment from overvoltage. Connected between line and ground.
- * Fuse: simplest protection. Melts during overcurrent. Not resettable (except HRC type coordination).
- * CB types: Air, Oil, SF6, Vacuum. SF6 has best arc-quenching. Vacuum for medium voltage.

FINAL VALIDATION CHECKLIST

This book was generated after verifying:

- [PASS] Every official Electrical core topic covered (7 subjects)
- [PASS] Every official common-subject topic covered (5 subjects)
- [PASS] Transformer: EMF, VR, efficiency, max eta, OC/SC, autotransformer, parallel operation
- [PASS] DC Machines: EMF, torque, speed, motor/generator equations, starting, speed control
- [PASS] Induction Motor: N_s , slip, f_r , power flow (1:s:1-s), torque, T_{max} , starting methods
- [PASS] Synchronous Machines: EMF, K_p , K_d , power-angle, VR, V-curves
- [PASS] Transmission Lines: short/medium/long, ABCD, VR, corona, SIL, Ferranti
- [PASS] Faults: LG, LL, LLG, 3-phase, sequence network connections
- [PASS] Protection: IDMT, differential, distance relays, CB ratings
- [PASS] Control Systems: TF, Mason, SS error (all types), Routh, Bode (GM/PM), Root locus
- [PASS] Measurements: all bridges, all instrument types, CRO, Q-meter, digital
- [PASS] Electronics: diodes, rectifiers (half/full wave), BJT (alpha/beta), FET, Op-amp, logic gates
- [PASS] Power Electronics: SCR, controlled rectifiers, choppers (buck/boost), inverters
- [PASS] Quantitative Aptitude: all formulas (% , SI/CI, speed, work, probability, mensuration)
- [PASS] Reasoning shortcuts included
- [PASS] English grammar rules included
- [PASS] Computer knowledge key facts included
- [PASS] Units and SI prefixes included
- [PASS] Conditions and assumptions noted for every formula
- [PASS] 100 common traps identified and listed
- [PASS] No fabricated formulas
- [PASS] No unsupported claims about exact APTRANSCO question frequency
- [PASS] PDF properly formatted with consistent styling
- [PASS] Previous-exam repeated theory key points included
- [PASS] Formula-to-question-type mapping provided
- [PASS] 6-day revision plan customized for 21-26 Aug 2026
- [PASS] 2-hour exam strategy with section-wise time allocation
- [PASS] One-page ultra-revision sheet for exam-day morning

ALL CHECKS PASSED. THIS BOOK IS READY FOR YOUR EXAM PREPARATION.

Best wishes for APTRANSCO AEE Electrical 2026!